
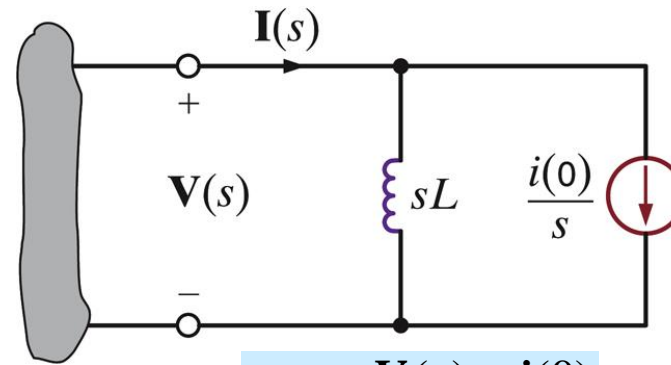
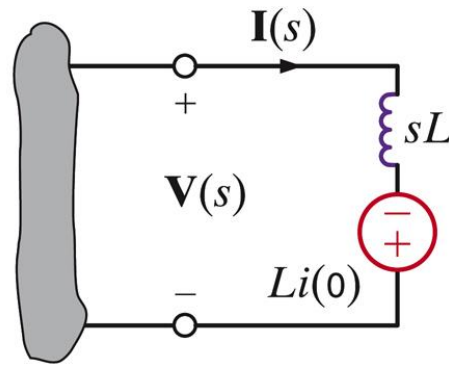


Inductor Models

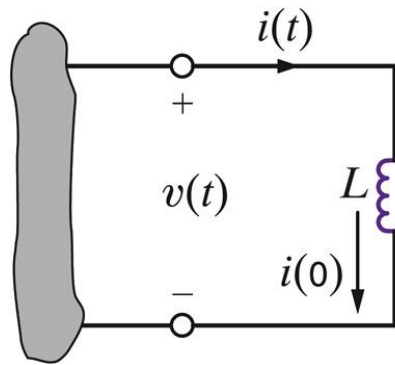

$$v(t) = L \frac{di}{dt}(t) \Rightarrow V(s) = L(sI(s) - i(0))$$

$$I(s) = \frac{V(s)}{Ls} + \frac{i(0)}{s}$$


$$\mathcal{L} \left[\frac{di}{dt} \right] = sI(s) - i(0)$$





LEARNING BY DOING

Determine the model in the s-domain and the expression for the voltage across the inductor

Steady state for $t < 0$

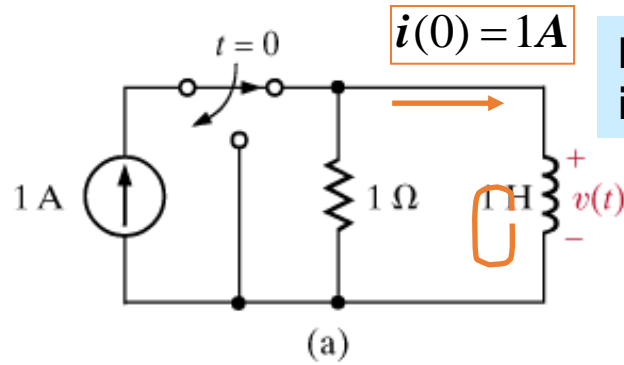

Inductor with initial current

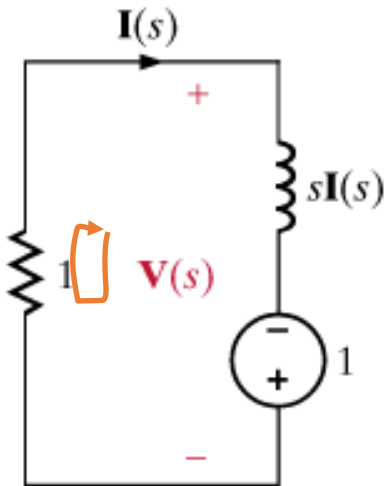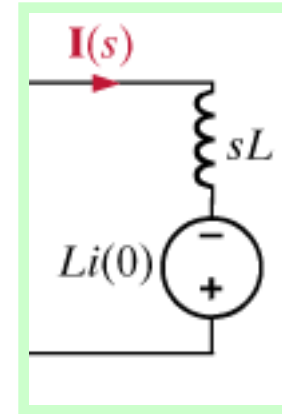

Equivalent circuit in s-domain

KVL: $1 = (1 + s)I(s)$

Ohm's Law

$$V(s) = -1 \times I(s) \Rightarrow V(s) = -\frac{1}{s + 1}$$



ANALYSIS TECHNIQUES


All the analysis techniques are applicable in the s-domain

LEARNING EXAMPLE

Draw the s-domain equivalent and find the voltage in both s-domain and time domain

$$I_S(s) = \frac{3}{s+1}$$


$$i_S(t) = 3e^{-t}u(t) \text{ mA}$$

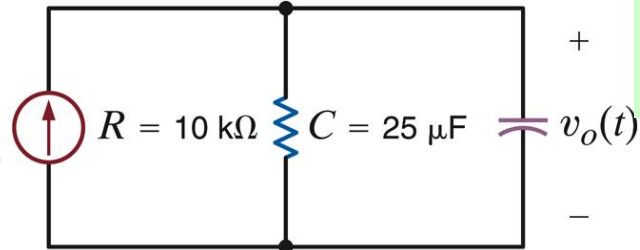

One needs to determine the initial voltage across the capacitor


$$i_S(t) = 0, t < 0 \Rightarrow v_o(0) = 0$$
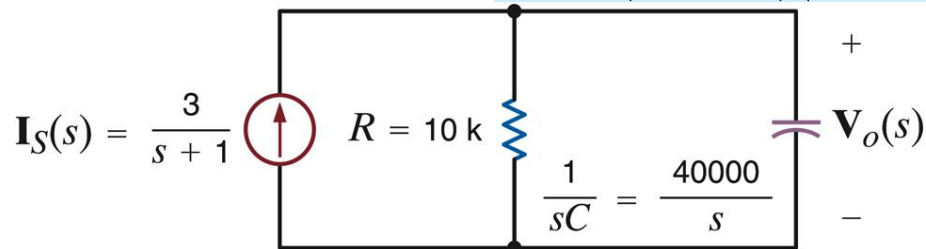
$$RC = (10 \times 10^3)(25 \times 10^{-6}) = 0.25$$



$$V_o(s) = \left(R \parallel \frac{1}{Cs} \right) I_S(s)$$
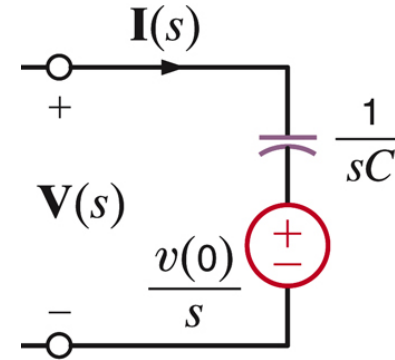
$$V_o(s) = \frac{R}{R + \frac{1}{Cs}} I_S(s) = \frac{1/C}{s + 1/RC} \times \frac{3 \times 10^{-3}}{s+1}$$



$$V_o(s) = \frac{120}{(s+4)(s+1)} = \frac{K_1}{s+4} + \frac{K_2}{s+1}$$

$$K_1 = (s+4)V_o(s) \Big|_{s=-4} = -40$$


$$K_2 = (s+1)V_o(s) \Big|_{s=-1} = 40$$

$$v_o(t) = 40[e^{-t} - e^{-4t}]u(t)$$

LEARNING EXAMPLE

Find $v_o(t)$ using node analysis, loop analysis, superposition, source transformation, Thevenin's and Norton's theorem.

Assume all initial conditions are zero

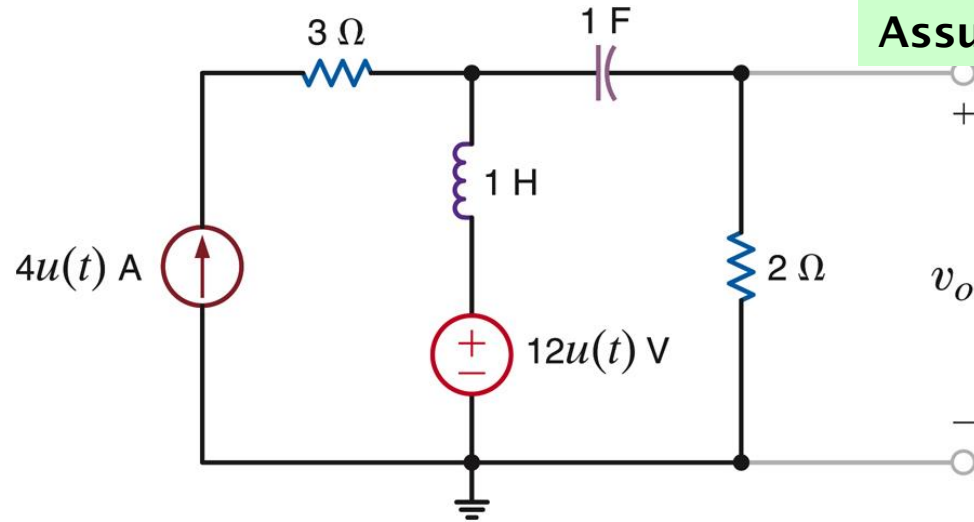

Node Analysis

$$\text{KCL @ } V_1 \quad \frac{V_1(s)}{2 + \frac{1}{s}} - \frac{4}{s} + \frac{V_1(s) - \frac{12}{s}}{s} + \frac{V_1(s) - V_o(s)}{\frac{1}{s}} = 0 \quad \times s$$



$$\text{KCL @ } V_o \quad \frac{V_o(s)}{2} + \frac{V_o(s) - V_1(s)}{\frac{1}{s}} = 0 \quad \times 2$$

Could have used voltage divider here


$$(1 + s^2)V_1(s) - s^2V_o(s) = \frac{4s + 12}{s} \quad \times 2s$$

$$-2sV_1(s) + (1 + 2s)V_o(s) = 0 \quad \times (1 + s^2)$$

$$V_o(s) = \frac{8(s + 3)}{(1 + s)^2}$$

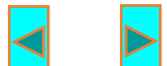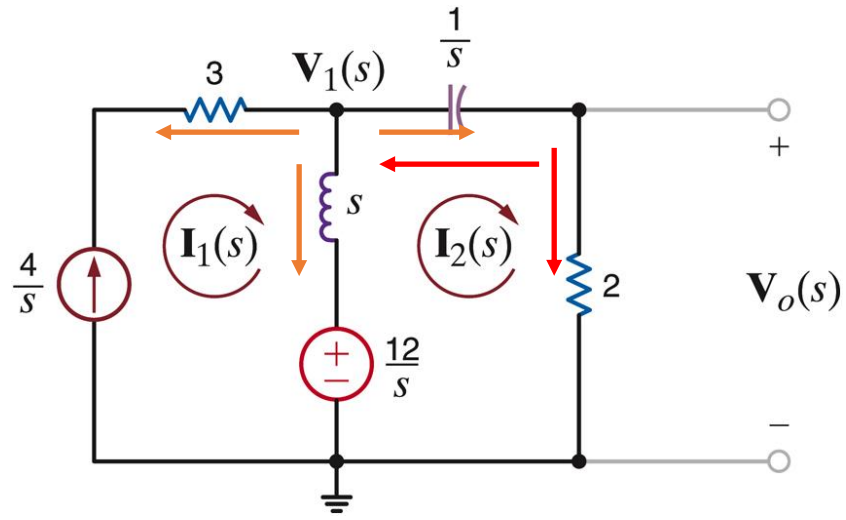

Loop Analysis

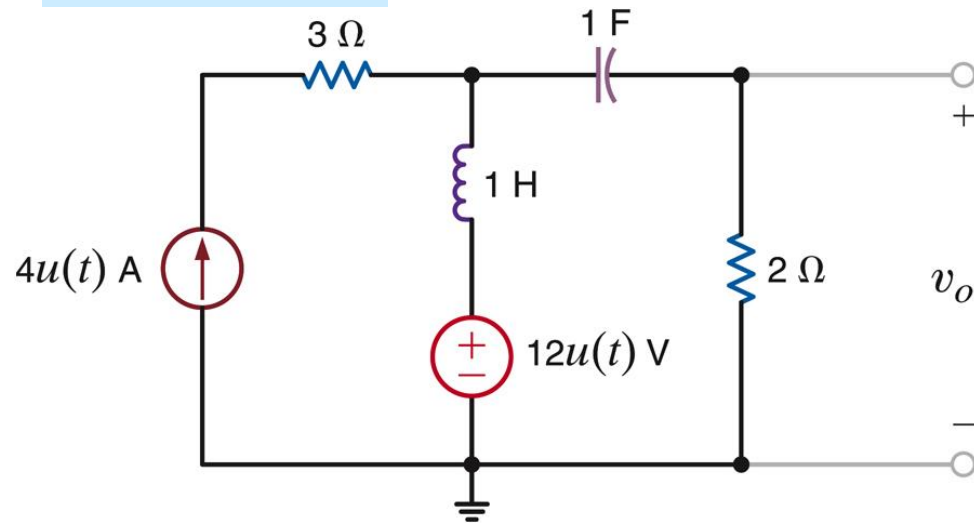

Loop 1


$$I_1(s) = \frac{4}{s}$$

Loop 2



$$s(I_2(s) - I_1(s)) + \frac{1}{s}I_2(s) + 2I_2(s) = \frac{12}{s}$$

$$I_2(s) = \frac{4(s+3)}{(s+1)^2}$$
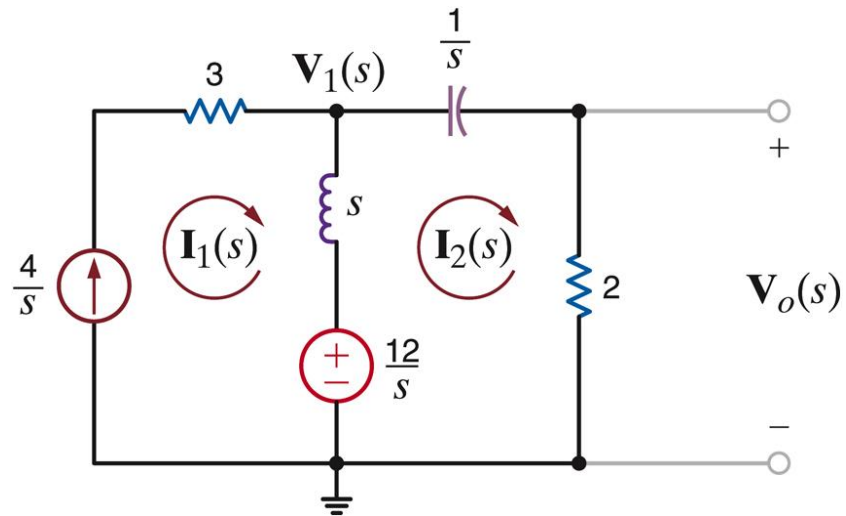
$$V_o(s) = 2I_2(s) = \frac{8(s+3)}{(s+1)^2}$$




Source Superposition

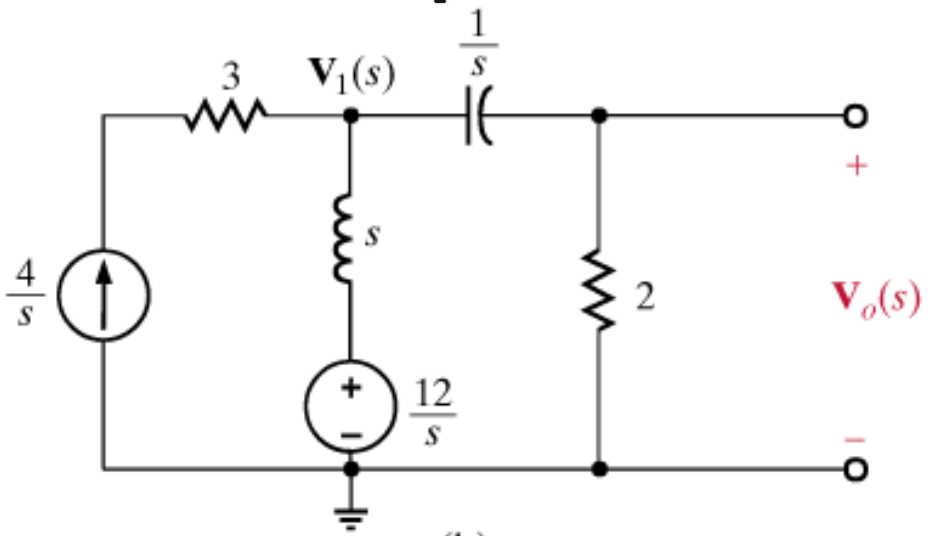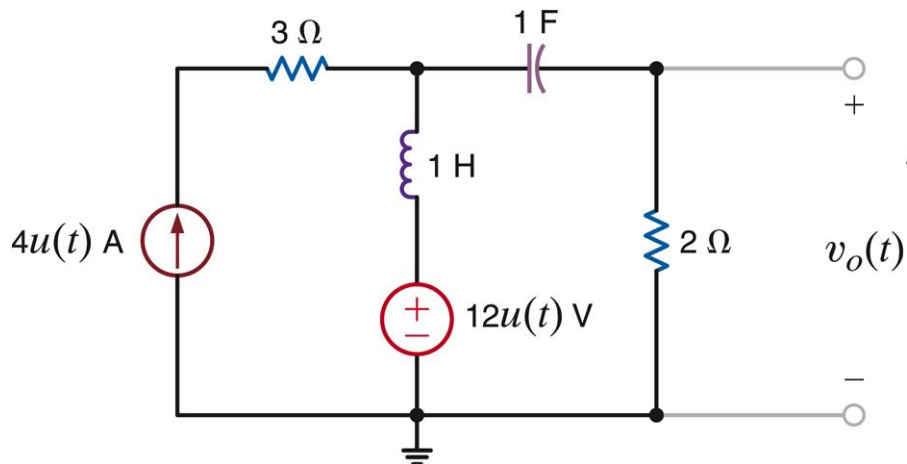


$$V_o(s) = V_o'(s) + V_o''(s) = \frac{8(s+3)}{(s+1)^2}$$

Applying current source

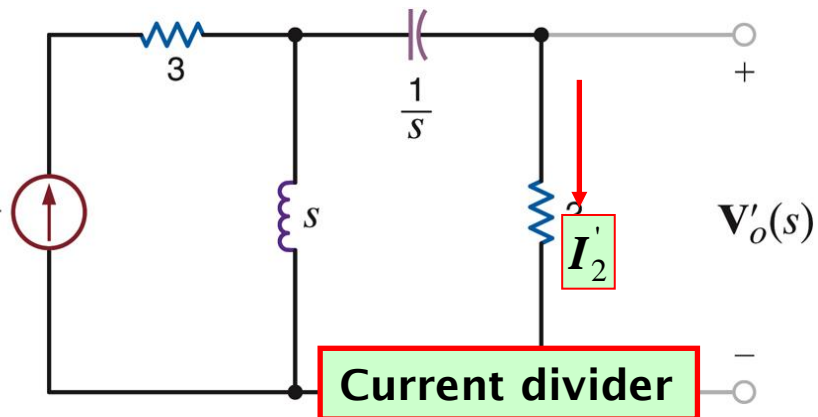

$$V_o'(s) = 2 \times \frac{s}{2 + \frac{1}{s} + s} \times \frac{4}{s}$$

Applying voltage source

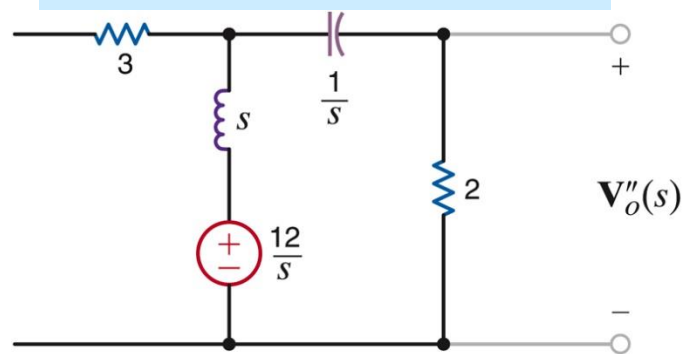


Voltage divider

$$V_o''(s) = \frac{2}{2 + \frac{1}{s} + s} \times \frac{12}{s}$$




Source Transformation

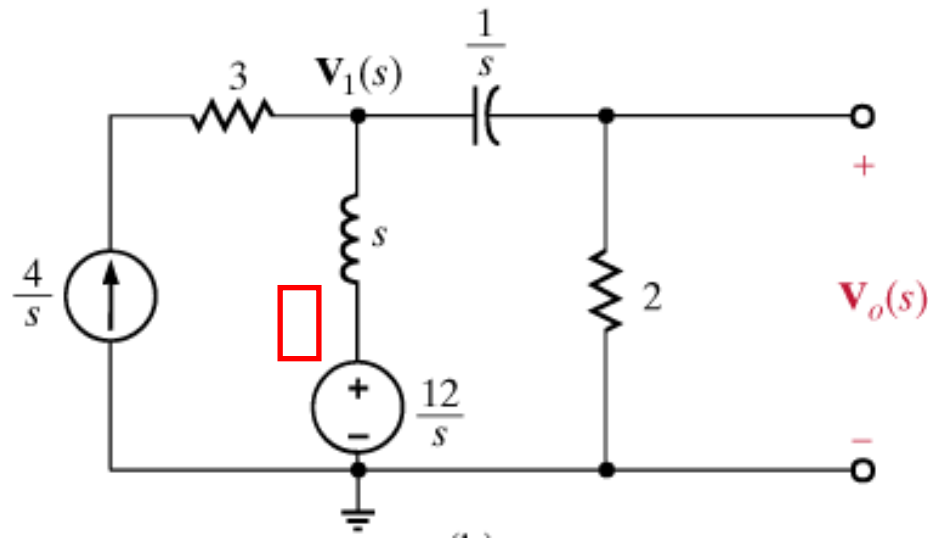

Combine the sources and use current divider

$$V_o(s) = 2 \times \frac{s}{s + \frac{1}{s} + 2} \left(\frac{4}{s} + \frac{12}{s^2} \right)$$

$$V_o(s) = \frac{8(s+3)}{(s+1)^2}$$


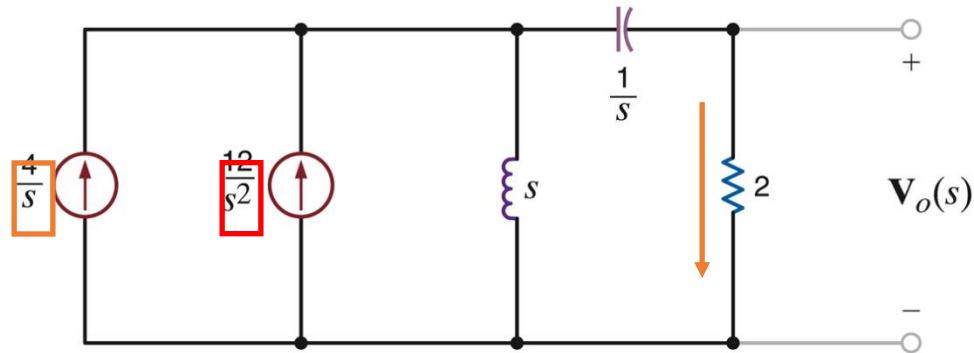


The resistance is redundant




Using Thevenin's Theorem

Reduce this part

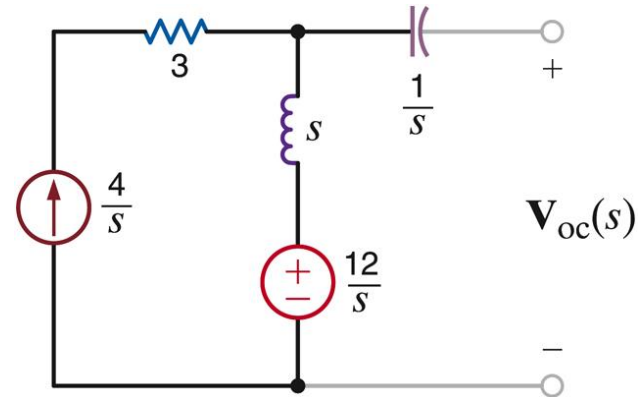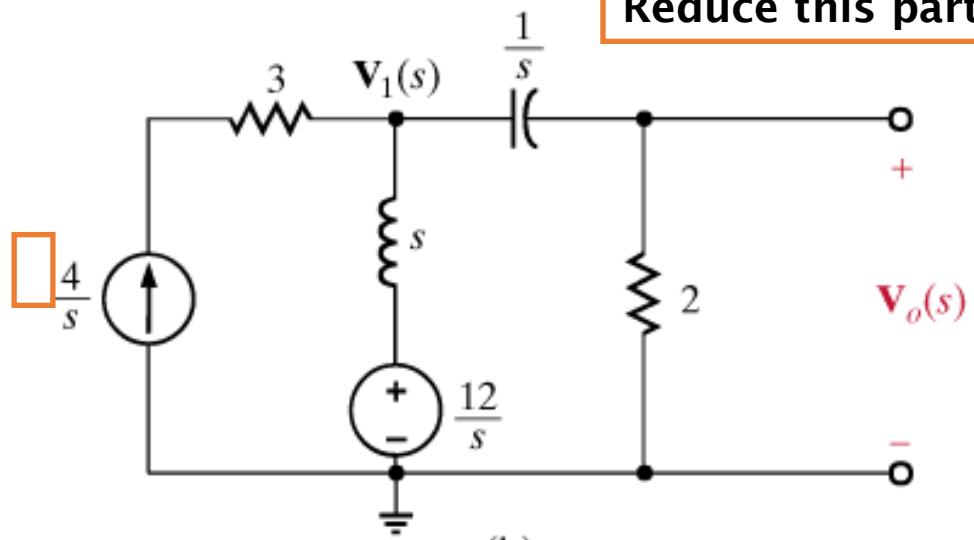


$$V_{OC}(s) = \frac{12}{s} + s \frac{4}{s} = \frac{4s + 12}{s}$$

Only independent sources

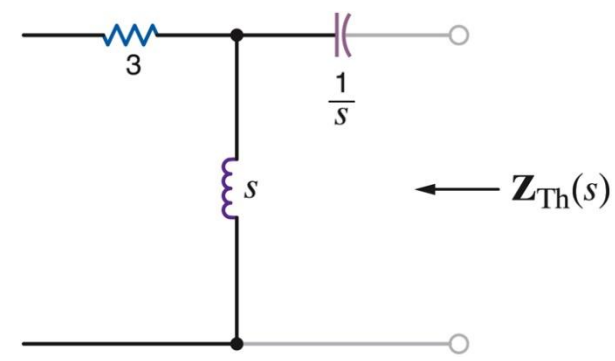
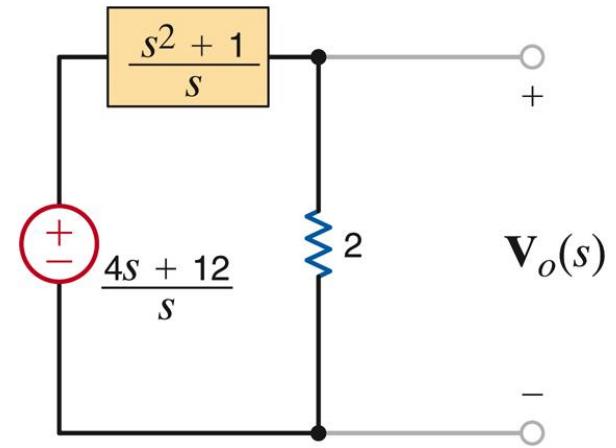
$$Z_{Th} = \frac{1}{s} + s = \frac{s^2 + 1}{s}$$



Voltage divider



$$V_o(s) = \frac{2}{2 + \frac{s^2 + 1}{s}} \frac{4s + 12}{s}$$

$$V_o(s) = \frac{8(s + 3)}{(s + 1)^2}$$




Using Norton's Theorem


Reduce this part

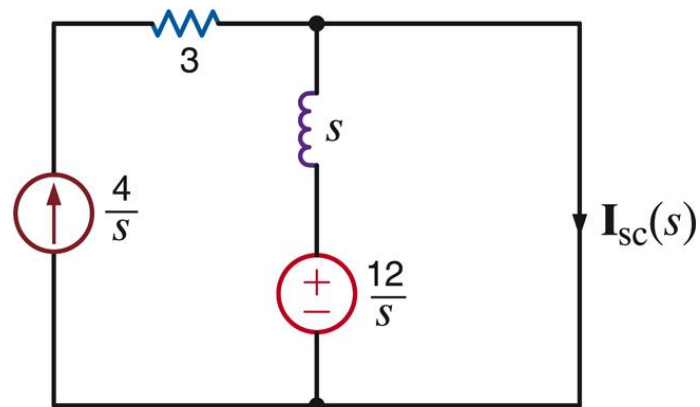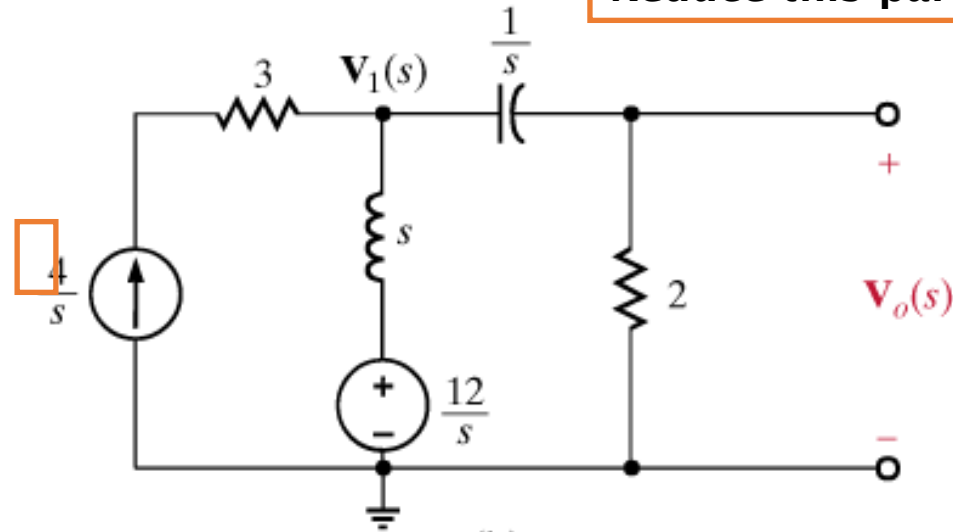
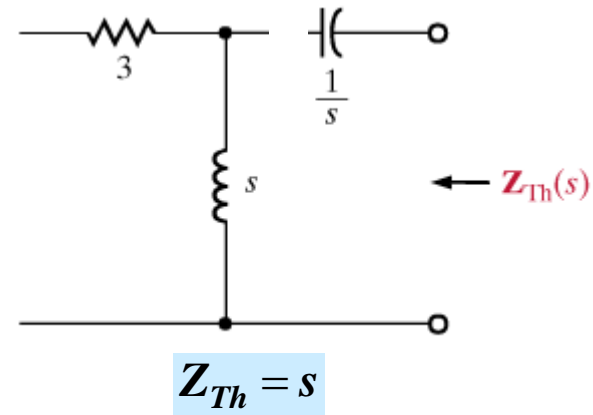
$$I_{sc}(s) = \frac{4}{s} + \frac{12/s}{s} = \frac{4s+12}{s^2}$$



$$Z_{Th} = s$$

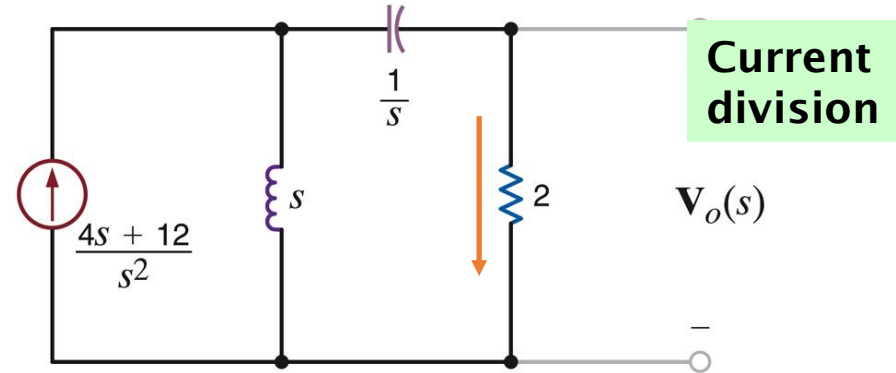


Current division

$$V_o(s) = 2 \times \frac{s}{s + \frac{1}{s} + 2} \frac{4s+12}{s^2}$$

$$V_o(s) = \frac{8(s+3)}{(s+1)^2}$$



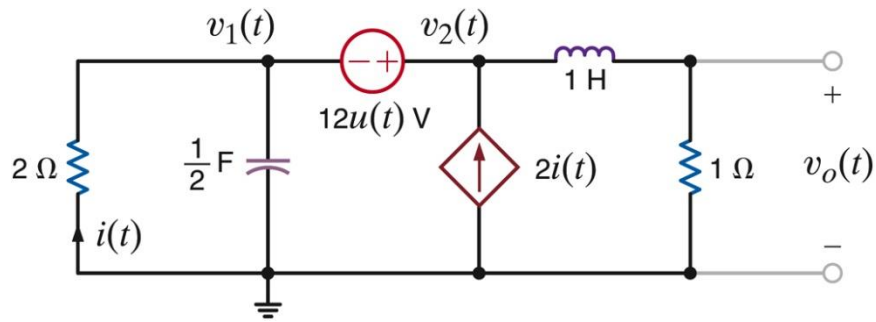
LEARNING EXAMPLE Determine the voltage $v_o(t)$. Assume all initial conditions to be zero



Selecting the analysis technique:

- Three loops, three non-reference nodes
- One voltage source between non-reference nodes - supernode
- One current source. One loop current known or supermesh
- If v_2 is known, v_o can be obtained with a voltage divider

Transforming the circuit to s-domain

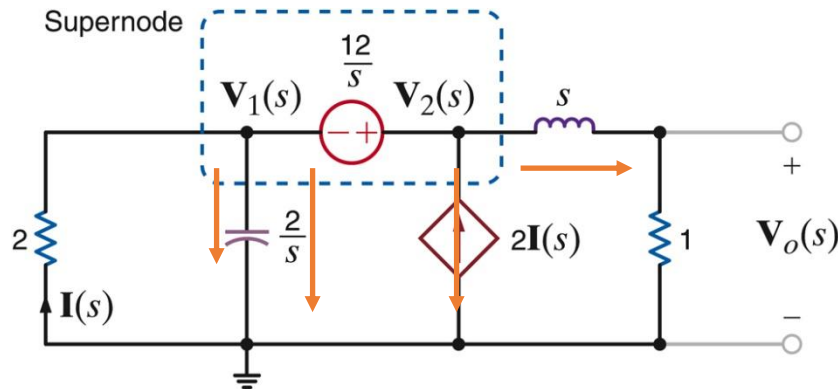

Doing the algebra: $V_1(s) = V_2(s) - 12/s$

$$I(s) = -V_2(s)/2 + 6/s$$

$$(1/2)(s+1)(V_2(s) - 12/s) - 2(-V_2(s)/2 + 6/s) + V_2(s)/(s+1) = 0$$

Supernode constraint: $V_2(s) - V_1(s) = \frac{12}{s}$

KCL@ supernode: $\frac{V_1(s)}{2} + \frac{V_1(s)}{2/s} - 2I(s) + \frac{V_2(s)}{s+1} = 0$

Controlling variable: $I(s) = -\frac{V_1(s)}{2}$

Voltage divider: $V_o(s) = \frac{1}{s+1} V_2(s)$

$$V_2(s) = \frac{12(s+1)(s+3)}{s(s^2+4s+5)}$$



$$V_o(s) = \frac{12(s+3)}{s(s^2+4s+5)}$$



Continued ...

Compute $V_o(s)$ using Thevenin's theorem

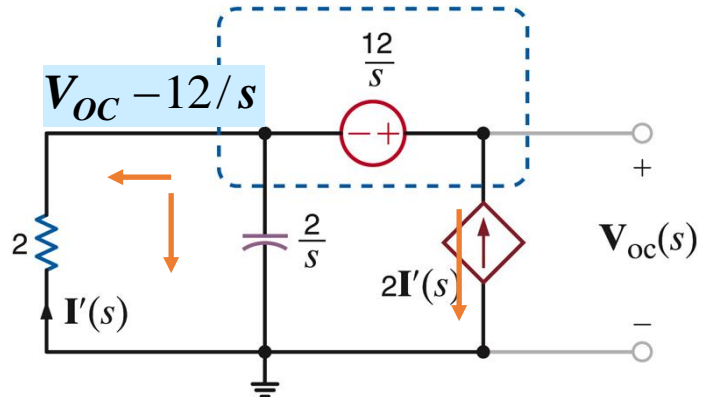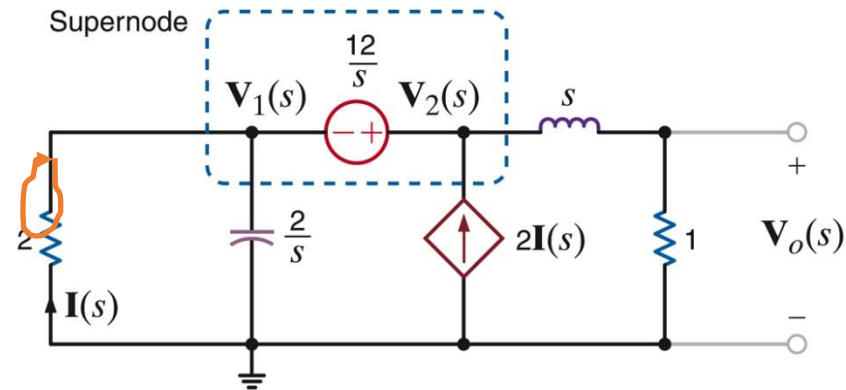
- keep dependent source and controlling variable in the same sub-circuit
- Make sub-circuit to be reduced as simple as possible
- Try to leave a simple voltage divider after reduction to Thevenin equivalent



$$\frac{V_{OC} - 12/s}{2} + \frac{V_{OC} - 12/s}{2/s} - 2I' = 0$$


$$I' = -\frac{V_{OC} - 12/s}{2} \quad V_{OC}(s) = \frac{12}{s}$$

$I' = 0$

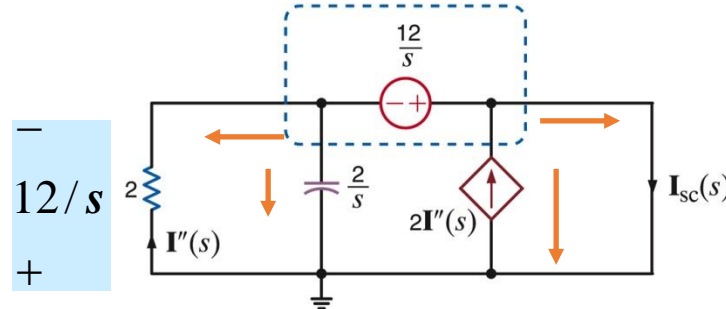

$$I_{SC} - 2I'' - I'' - 2I''/(2/s) = 0 \quad I'' = 6/s$$
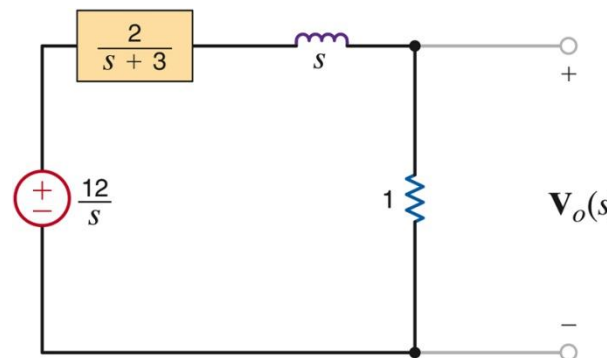
$$I_{SC} = \frac{6(s+3)}{s} \quad Z_{TH} = \frac{V_{OC}(s)}{I_{SC}(s)} = \frac{2}{s+3}$$



$$V_o(s) = \frac{1}{1 + s + \frac{2}{s+3}} \times \frac{12}{s}$$