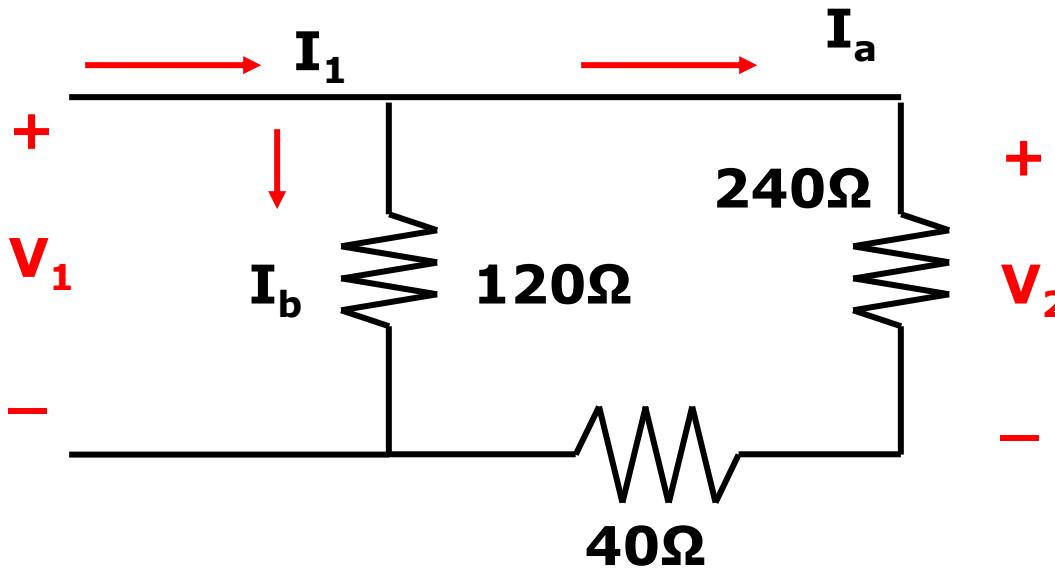


Solution

i) $I_2 = 0$ (open circuit port 2). Redraw the circuit.



$$V_1 = 120I_b \dots\dots(1)$$

$$I_b = \frac{280}{400} I_1 \dots\dots(2)$$

sub (1) \rightarrow (2)

$$\therefore Z_{11} = \frac{V_1}{I_1} = 84\Omega$$


$$V_2 = 240I_a \dots\dots(3)$$

$$I_a = \frac{120}{400} I_1 \dots\dots(4)$$

sub (4) \rightarrow (3)

$$\therefore Z_{21} = \frac{V_2}{I_1} = 72\Omega$$

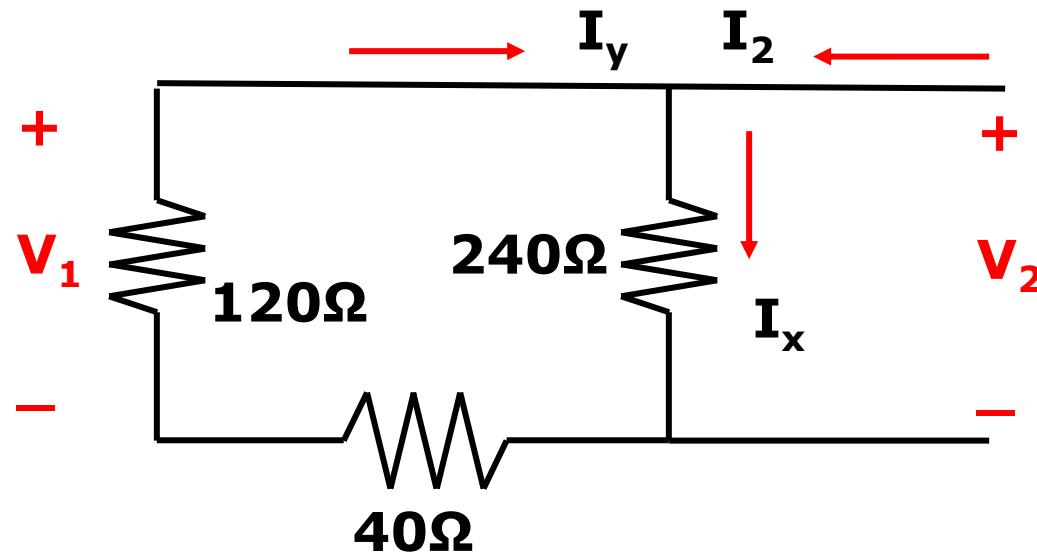ii) $I_1 = 0$ (open circuit port 1). Redraw the circuit.



$$V_2 = 240I_x \dots\dots(1)$$

$$I_x = \frac{160}{400} I_2 \dots\dots(2)$$

sub (1) \rightarrow (2)

$$\therefore Z_{22} = \frac{V_2^2}{I_2} = 96\Omega$$

$$V_1 = 120I_y \dots\dots(3)$$

$$I_y = \frac{240}{400} I_2 \dots\dots(4)$$

sub (4) \rightarrow (3)

$$\therefore Z_{12} = \frac{V_1}{I_2} = 72\Omega$$

In matrix form:

$$[Z] = \begin{bmatrix} 84 & 72 \\ 72 & 96 \end{bmatrix}$$

EXAMPLE 13.1 Find the Z-parameters of the two-port circuit in Fig. 13-2.

Apply KVL around the two loops in Fig. 13-2 with loop currents \mathbf{I}_1 and \mathbf{I}_2 to obtain

$$\begin{aligned}\mathbf{V}_1 &= 2\mathbf{I}_1 + \mathbf{s}(\mathbf{I}_1 + \mathbf{I}_2) = (2 + \mathbf{s})\mathbf{I}_1 + \mathbf{s}\mathbf{I}_2 \\ \mathbf{V}_2 &= 3\mathbf{I}_2 + \mathbf{s}(\mathbf{I}_1 + \mathbf{I}_2) = \mathbf{s}\mathbf{I}_1 + (3 + \mathbf{s})\mathbf{I}_2\end{aligned}\tag{3}$$

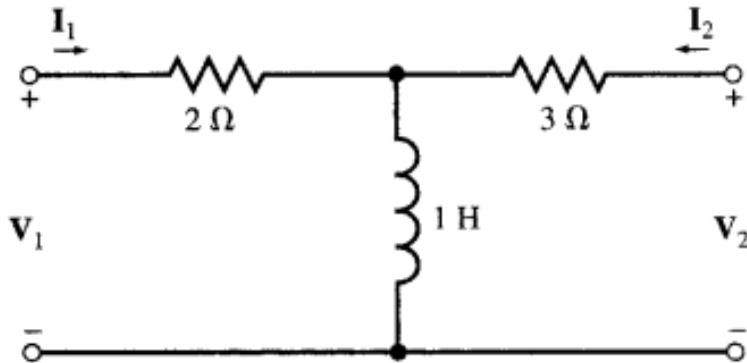


Fig. 13-2


By comparing (1) and (3), the Z-parameters of the circuit are found to be

$$\begin{aligned}\mathbf{Z}_{11} &= \mathbf{s} + 2 \\ \mathbf{Z}_{12} &= \mathbf{Z}_{21} = \mathbf{s} \\ \mathbf{Z}_{22} &= \mathbf{s} + 3\end{aligned}\tag{4}$$

Note that in this example $\mathbf{Z}_{12} = \mathbf{Z}_{21}$.

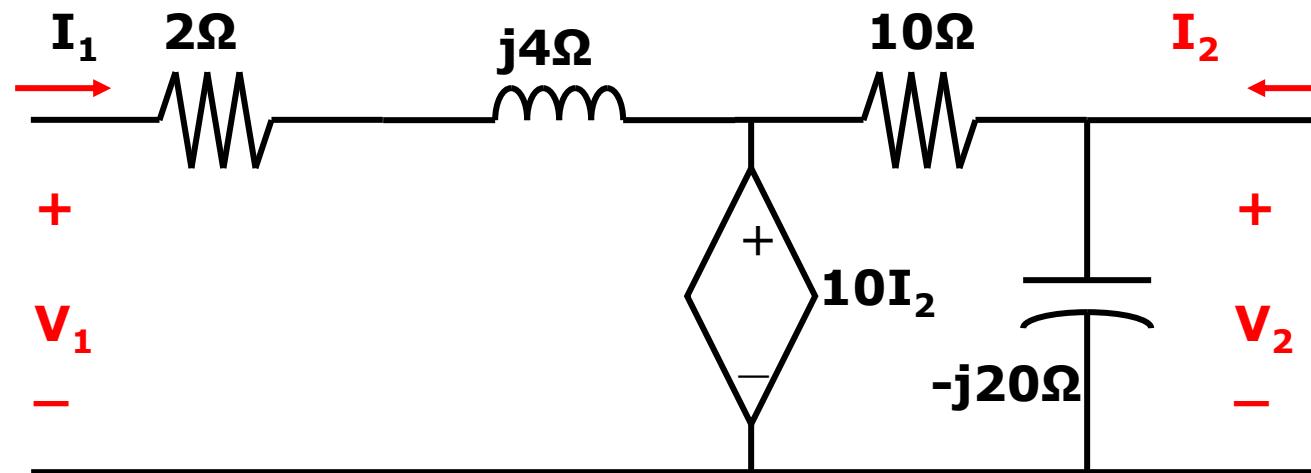
Example 2

Find the Z – parameter of the circuit below



Solution

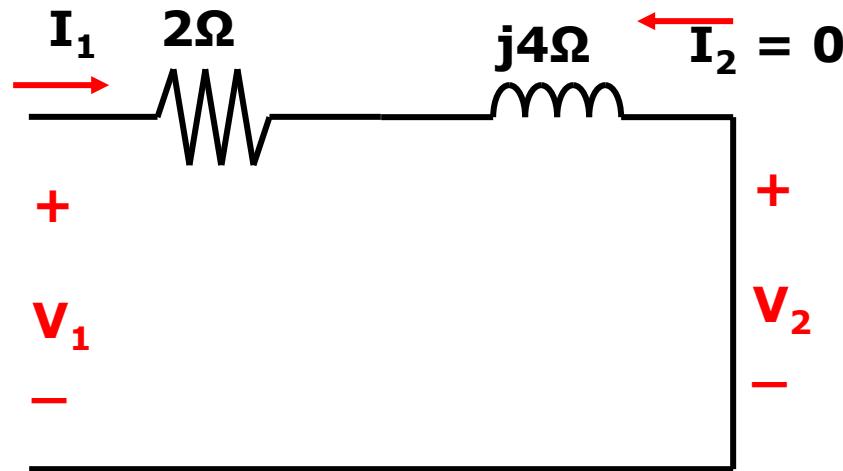i) $I_2 = 0$ (open circuit port 2). Redraw the circuit.




$$V_1 = I_1 (2 + j4)$$

$$\therefore Z_{11} = \frac{V_1}{I_1} = (2 + j4)\Omega$$

$$V_2 = 0 \text{ (short circuit)}$$

$$\therefore Z_{21} = 0\Omega$$

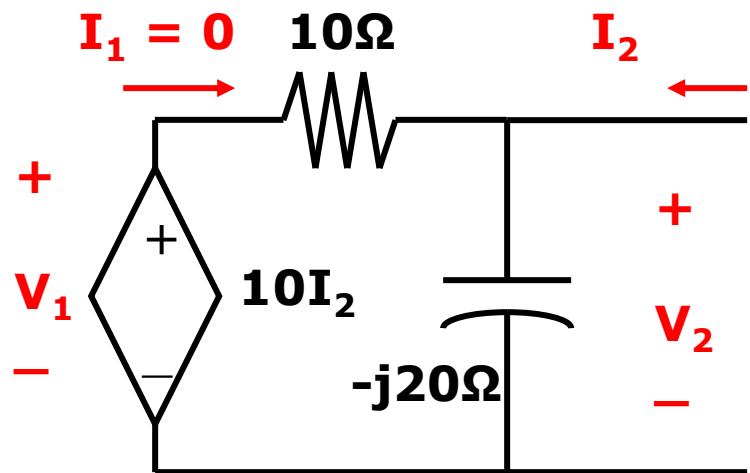ii) $I_1 = 0$ (open circuit port 1). Redraw the circuit.



In matrix form;

$$[Z] = \begin{bmatrix} (2 + j4) & 0 \\ 10 & (16 - j8) \end{bmatrix}$$

$$V_1 = 10I_2$$

$$\therefore Z_{12} = \frac{V_1}{I_2} = 10\Omega$$


$$I_2 = \frac{V_2}{-j20} + \frac{V_2 - 10I_2}{10}$$

$$2I_2 = V_2 \left(\frac{j}{20} + \frac{1}{10} \right)$$

$$\therefore Z_{22} = \frac{V_2}{I_2} = (16 - j8)\Omega$$

Y - PARAMETER

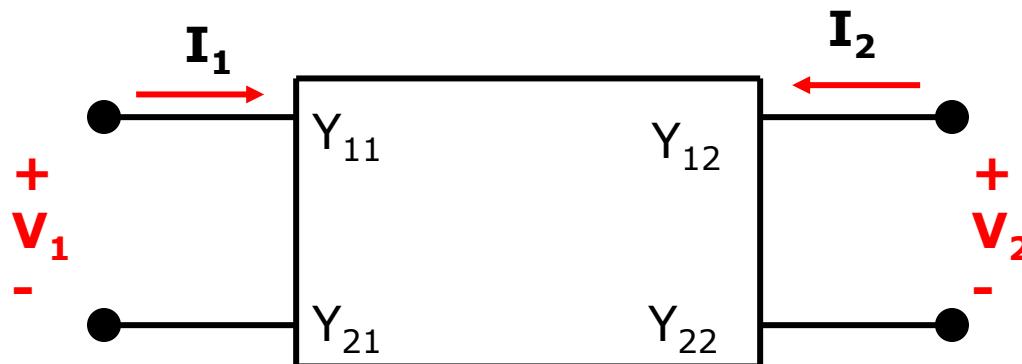- Y – parameter also called admittance parameter and the units is siemens (S).
- The “black box” that we want to replace with the Y-parameter is shown below.



- The terminal current can be expressed in term of terminal voltage as:

$$I_1 = y_{11}V_1 + y_{12}V_2 \quad \text{--- (1)}$$

$$I_2 = y_{21}V_1 + y_{22}V_2 \quad \text{--- (2)}$$

- In matrix form:

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$