



# **VLSI Design (BEC-41)**

## **(Unit-2, Lecture-2)**




**Presented By:**  
**Prof. R. K. Chauhan**

**Department of Electronics and Communication Engineering**


 
# MOS INVERTER


- Inverter is fundamental logic gate uses single input.
- Basic principles employing in design and analysis of inverter can be directly applied on complex gates.
- Therefore, inverter design forms basis for digital circuits.
- First we start with DC Characteristics. The DC response is Ultra Low Frequency response of the Circuit.
- When you are at a logic low or high before switching, it is a DC condition.
- The transient can be thought of as a perturbation of the DC Since valid logic levels are a range of voltages, it is a tolerant system.



Symbol

A	B
0	1
1	0


Truth Table

 

**Fig.** Voltage transfer characteristic (VTC) of the ideal inverter




## Noise Immunity and Noise Margins

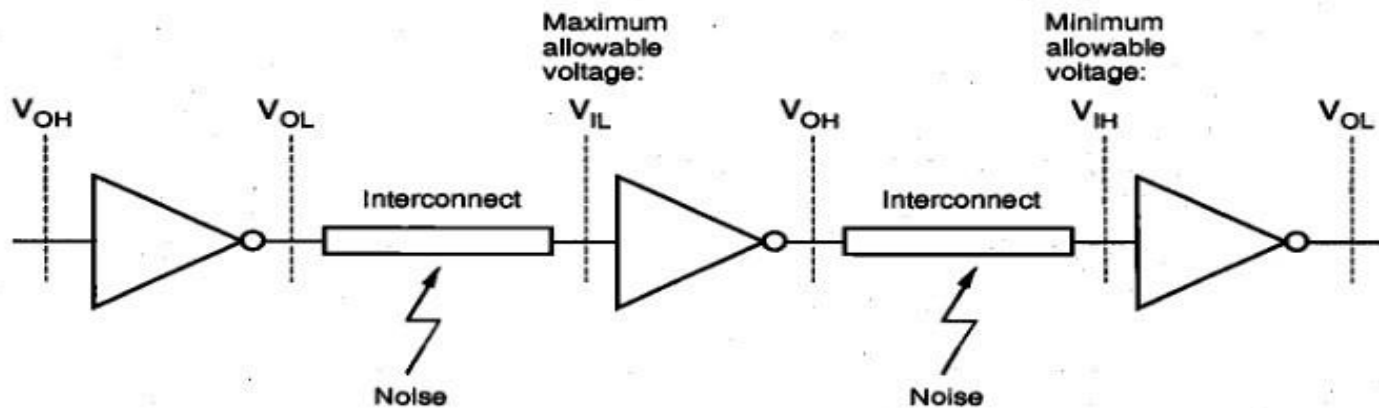

- Output signal is transmitted through interconnect to next inverter.
- Interconnects are prone to noise. Suppose output of 1<sup>st</sup> inverter is perturbed to a level higher than  $V_{IL}$ . Then this can not predict correct output of 2<sup>nd</sup> inverter.
- Thus,  $V_{IL}$  is maximum allowable input voltage which is low enough to ensure '1' output.
- Similarly argument for  $V_{IH}$ .
- Noise tolerance or Noise Margins and denoted by NM. Two noise margins will be defined for low signal level as  $NM_L$  and high signal level as  $NM_H$



# Noise Immunity and Noise Margins

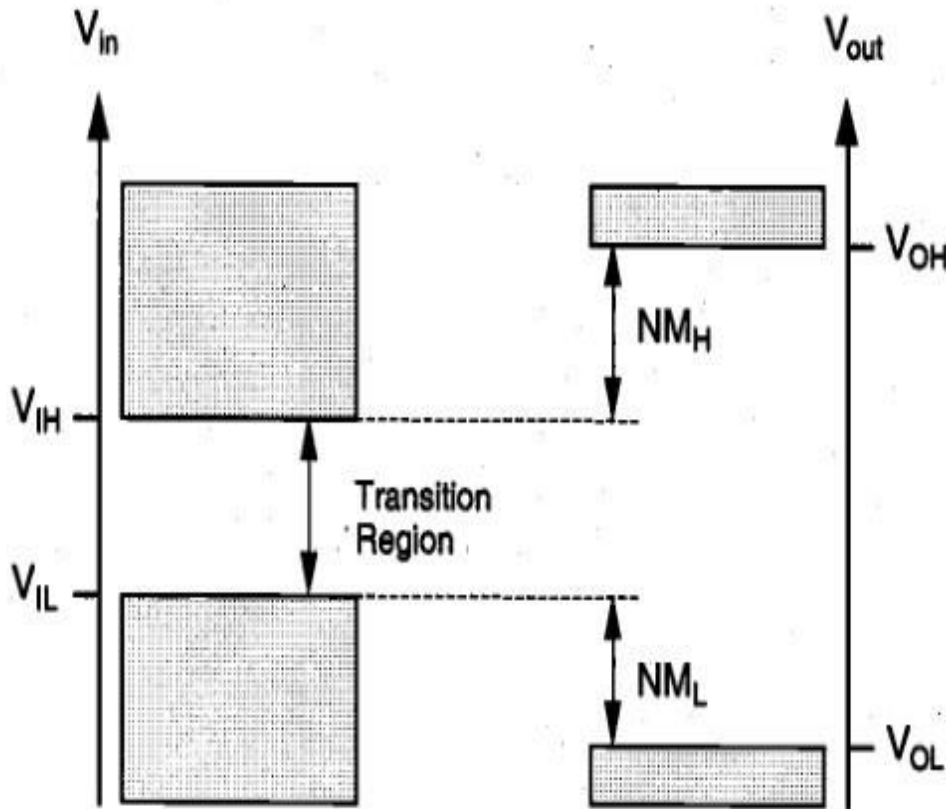

$$N_{ML} = V_{IL} - V_{OL}$$

$$N_{MH} = V_{OH} - V_{IH}$$

- Noise tolerance or Noise Margins and denoted by NM.
- Two noise margins will be defined for low signal level as  $NM_L$  and high signal level as  $NM_H$



## Noise Immunity and Noise Margins

- If the input signal is perturbed from its nominal value because of external influences, such as noise:

$$V_{out}' = f(V_{in} + \Delta V_{noise})$$

$$V_{out}' = f(V_{in}) + \frac{dV_{out}}{dV_{in}} \cdot \Delta V_{noise} + \text{higher order terms (neglected)}$$

**Perturbed Output = Nominal Output + Gain x External Perturbation**

- If the magnitude of the voltage gain at the nominal input voltage  $V_{in}$  is smaller than unity, then the input perturbation is not amplified and, consequently, the output perturbation remains relatively small.
- Otherwise, with the voltage gain larger than unity, a small perturbation in the input voltage level will cause a rather large perturbation in the output voltage.
- Hence, we define the boundaries of the valid input signal regions as the voltage points where the magnitude of the inverter voltage gain is equal to unity.



# Noise Immunity and Noise Margins

## Critical Parameters for Inverter design:

$V_{OH}$ : Maximum output voltage when the output level is logic " 1 "

$V_{OL}$ : Minimum output voltage when the output level is logic "0"

$V_{IL}$ : Maximum input voltage which can be interpreted as logic "0"

$V_{IH}$ : Minimum input voltage which can be interpreted as logic " 1 "



## Power and Area Consideration

- The DC power dissipation of an inverter is defined as

$$P_{DC} = V_{DD} \cdot I_{DC}$$

- Current depends upon input and output voltage levels. Assume input voltage level 50% is at logic '0' and 50% at logic '1'.

$$P_{DC} = \frac{V_{DD}}{2} \cdot [I_{DC}(V_{in} = low) + I_{DC}(V_{in} = high)]$$

- To reduce chip area, one has to reduce the size of transistor i.e. gate area ( $W \times L$ ). Thus keep  $W/L$  ratio close to unity.




## **Inverters with different types of load**

- 1. Resistive-Load Inverter**
- 2. Depletion-load NMOS Inverter**
- 3. Enhancement-load NMOS Inverter**
- 4. CMOS Inverter**





## Resistive-Load Inverter

 


- The average DC power consumption of the resistive-load inverter circuit is found by considering two cases,  $V_{in} = V_{OL}$  (Low) and  $V_{in} = V_{OH}$  (high).
- When the input voltage is equal to  $V_{OL}$ , the driver transistor is in cut-off. Consequently, there is no steady-state current flow in the circuit ( $I_D = I_R = 0$ ), and the DC power dissipation is equal to zero.
- When the input voltage is equal to  $V_{OH}$  on the other hand, both the driver MOSFET and the load resistor conduct a nonzero current. Since the output voltage in this case is equal to  $V_{OL}$
- The current drawn from the power supply can be found as:

$$I_D = I_R = \frac{V_{DD} - V_{OL}}{R_L}$$

- The chip area occupied by the resistive-load inverter circuit depends on two parameters, the  $(W/L)$  ratio of the driver transistor and the value of the resistor  $R_L$ . The area of the driver transistor can be approximated by the gate area,  $(W \times L)$ .



# Resistive-Load Inverter

 

**Table:** Operating regions of the driver transistor in the resistive-load inverter.

Input Voltage Range	Operating Mode
$V_{in} < V_{T0}$	cut-off
$V_{T0} \leq V_{in} < V_{out} + V_{T0}$	saturation
$V_{in} \geq V_{out} + V_{T0}$	linear



# Resistive-Load Inverter

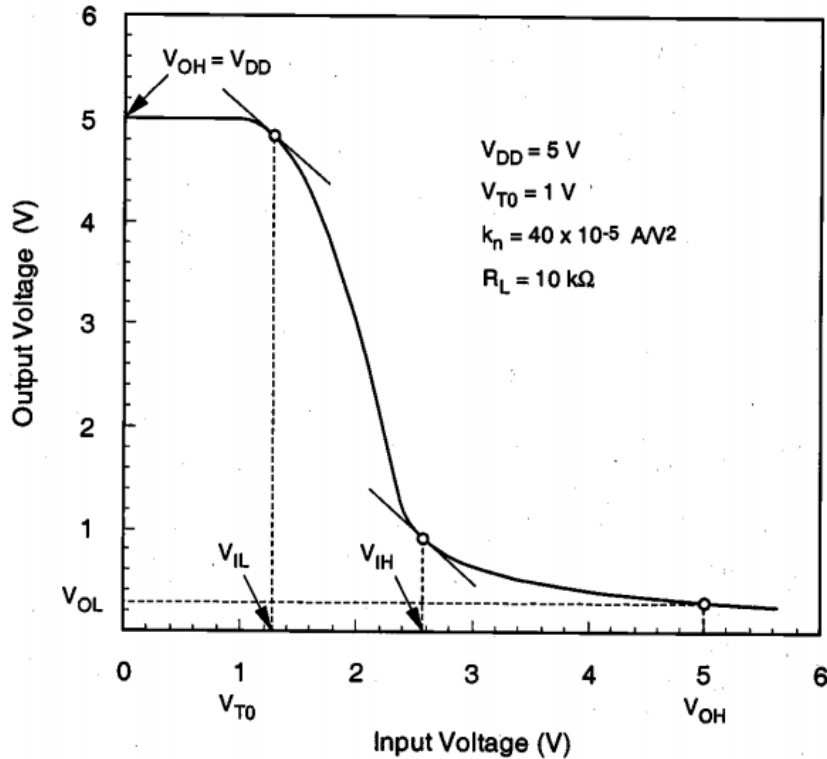


Fig. Typical VTC of a resistive-load inverter circuit.


 


Fig. Voltage transfer characteristics of the resistive-load inverter, for different value of the parameter ( $k_n$ ,  $R_L$ )

 

## Depletion-load NMOS Inverter




- Several disadvantages of the enhancement-type load inverter can be avoided by using a depletion-type nMOS transistor as the load device.-
- The fabrication process for producing an inverter with an enhancement-type nMOS driver and a depletion-type nMOS load is slightly more complicated and requires additional processing steps, especially for the channel implant to adjust the threshold voltage of the load device.


- The resulting improvement of circuit performance and integration possibilities, however, easily justify the additional processing effort required for the fabrication of depletion-load inverters.
- The immediate advantages of implementing this circuit configuration are:
  - (i) Sharp VTC transition and better noise margins,
  - (ii) single power supply, and
  - (iii) smaller overall layout area.



## Depletion-load NMOS Inverter

 

(a)

 

(b)

**Fig.(a)** Inverter circuit with saturated enhancement-type nMOS load. **(b)** Inverter with linear enhancement-type load.

- The circuit configurations of two inverters with enhancement-type load devices are depending on the bias voltage applied to its gate terminal, the load transistor can be operated either in the saturation region or in the linear region.



## Depletion-load NMOS Inverter (Continued..)

- Both types of inverters have some distinct advantages and disadvantages from the circuit design point of view.
- The saturated enhancement-load inverter shown in Fig.(a) requires a single voltage supply and a relatively simple fabrication process, yet the  $V_{OH}$  level is limited to  $(V_{DD} - V_{Tload})$
- The load device of the inverter circuit shown in Fig. (b), on the other hand, is always biased in the linear region. Thus, the  $V_{OH}$  level is equal to  $V_{DD}$ , resulting in higher noise margins compared to saturated enhancement-load inverter.
- The most significant drawback of this configuration is the use of two separate power supply voltages.
- In addition, both types of inverter circuits suffer from relatively high stand-by (DC) power dissipation
- Hence, enhancement-load nMOS inverters are not used in any large-scale digital applications.




## CMOS Inverter


- The CMOS inverter has two important advantages over the other inverter configurations:
- The first and perhaps the most important advantage is that the steady-state power dissipation of the CMOS inverter circuit is virtually negligible, except for small power dissipation due to leakage currents. In all other inverter structures examined so far, a nonzero steady-state current is drawn from the power source when the driver transistor is turned on, which results in a significant DC power consumption.
- The other advantages of the CMOS configuration are that the voltage transfer characteristic (VTC) exhibits a full output voltage swing between 0 V and  $V_{DD}$ , and that the VTC transition is usually very sharp. Thus, the VTC of the CMOS inverter resembles that of an ideal inverter.



# CMOS Inverter

 

(a)

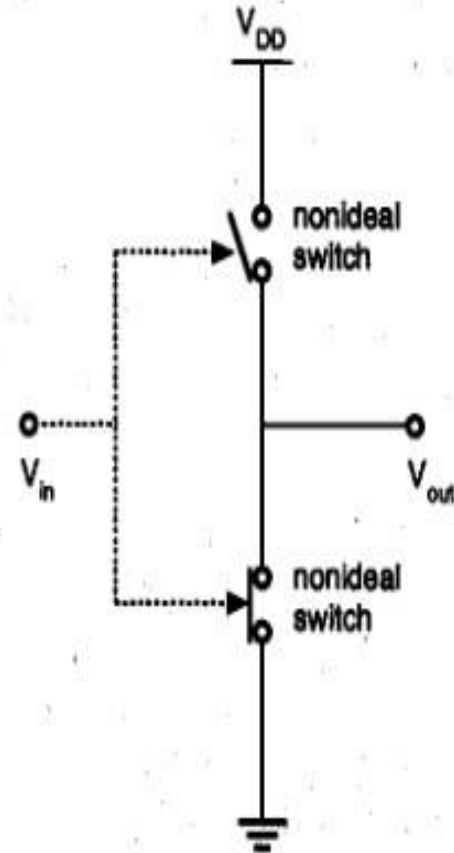

(b)





# CMOS Inverter

 


Fig. VTC Characteristic

A: P Linear N Cut-off

B: P Linear N Saturation

C: P saturation N Saturation

D: P Saturation N Linear

E: P Cut-off N Linear

$$\frac{k_n}{k_p} = \frac{\mu_n C_{ox} \cdot \left(\frac{W}{L}\right)_n}{\mu_p C_{ox} \cdot \left(\frac{W}{L}\right)_p} = \frac{\mu_n \cdot \left(\frac{W}{L}\right)_n}{\mu_p \cdot \left(\frac{W}{L}\right)_p}$$

For Symmetric Inverter:

$$V_{T0} = V_{T0n} = -V_{T0p} \text{ and } K_R = 1$$

$$\left(\frac{W}{L}\right)_n = \frac{\mu_p}{\mu_n} \approx \frac{230 \text{ cm}^2/\text{V}\cdot\text{s}}{580 \text{ cm}^2/\text{V}\cdot\text{s}}$$

$$\left(\frac{W}{L}\right)_p \approx 2.5 \left(\frac{W}{L}\right)_n$$