


- The y-parameter that we want to determine are  $Y_{11}$ ,  $Y_{12}$ ,  $Y_{21}$ ,  $Y_{22}$ . The values of the parameters can be evaluate by setting:
  - i)  $V_1 = 0$  (input port short – circuited).
  - ii)  $V_2 = 0$  (output port short – circuited).
- Thus;

$$Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} \quad Y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0}$$

$$Y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} \quad Y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0}$$

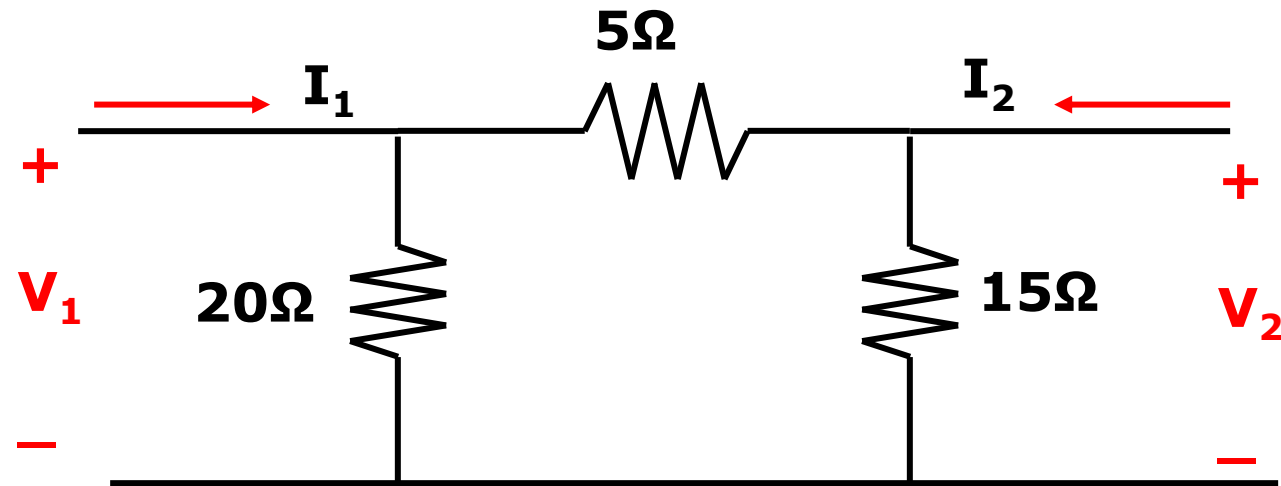
# Example 1

Find the Y – parameter of the circuit shown below.



# Solution

i)  $V_2 = 0$

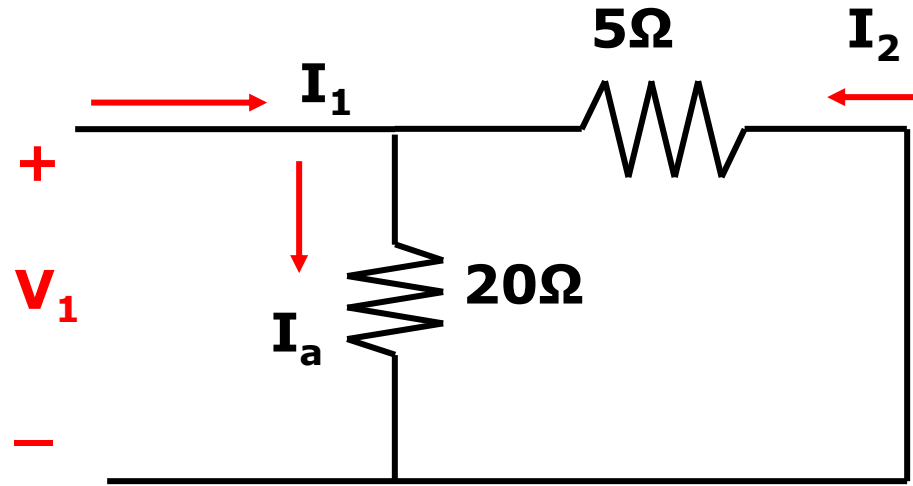

$$V_1 = 20I_a \dots \dots (1)$$

$$I_a = \frac{5}{25} I_1 \dots \dots (2)$$


sub (1)  $\rightarrow$  (2)

$$\therefore Y_{11} = \frac{I_1}{V_1} = \frac{1}{4} S$$

$$V_1 = -5I_2$$

$$\therefore Y_{21} = \frac{I_2}{V_1} = -\frac{1}{5} S$$

ii)  $V_1 = 0$

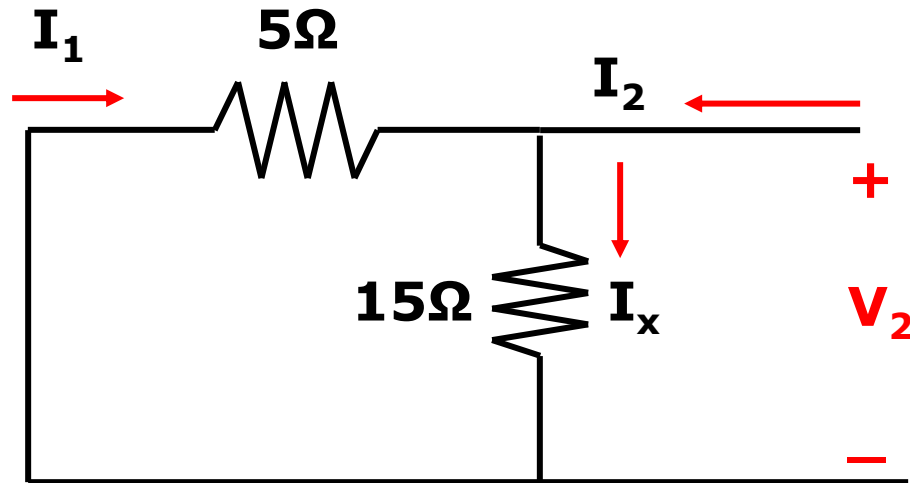

In matrix form;

$$[Y] = \begin{bmatrix} \frac{1}{4} & -\frac{1}{5} \\ -\frac{1}{5} & \frac{4}{15} \end{bmatrix} S$$

$$V_2 = 15I_x \dots \dots (3)$$

$$I_x = \frac{5}{25} I_2 \dots \dots (4)$$

sub (3)  $\rightarrow$  (4)


$$\therefore Y_{22} = \frac{I_2}{V_2} = \frac{4}{15} S$$

$$V_2 = -5I_1$$

$$\therefore Y_{12} = \frac{I_1}{V_2} = -\frac{1}{5} S$$

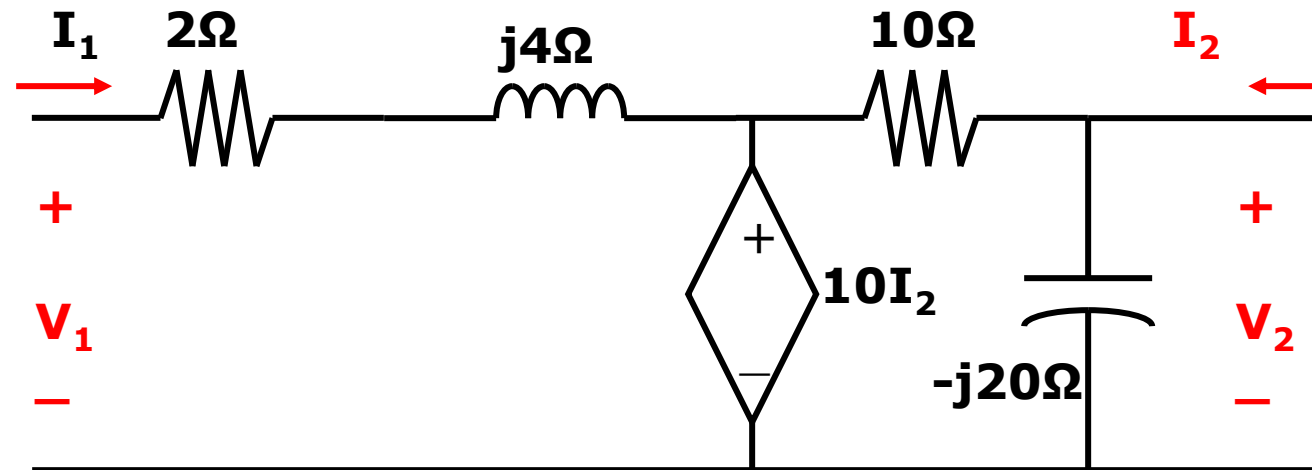
## Example 2 (circuit with dependent source)

Find the Y – parameters of the circuit shown.



# Solution

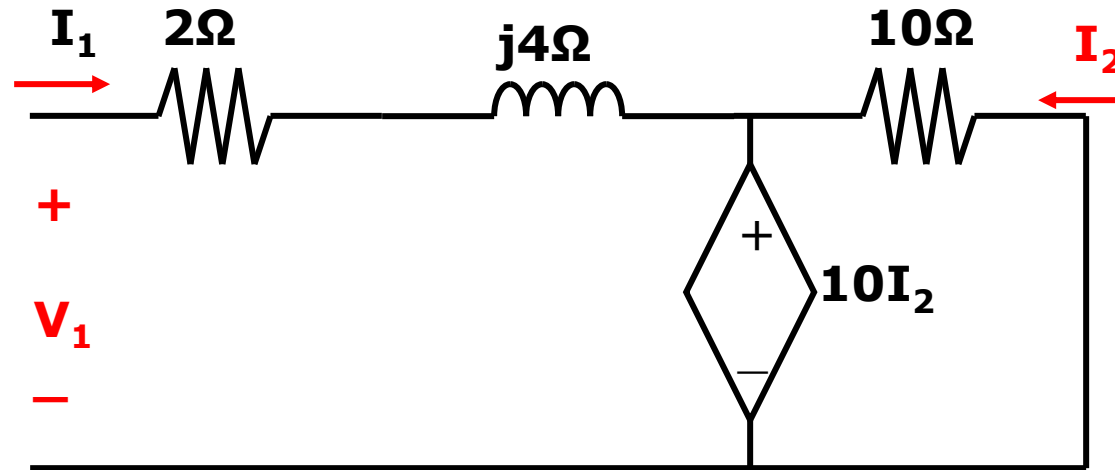i)  $V_2 = 0$  (short – circuit port 2). Redraw the circuit.




$$I_2 = 0$$

$$V_1 = (2 + j4)I_1$$

$$\therefore Y_{11} = \frac{I_1}{V_1} = \frac{1}{2 + j4} = (0.1 - j0.2) \text{ S}$$

$$\therefore Y_{21} = \frac{I_2}{V_1} = 0 \text{ S}$$

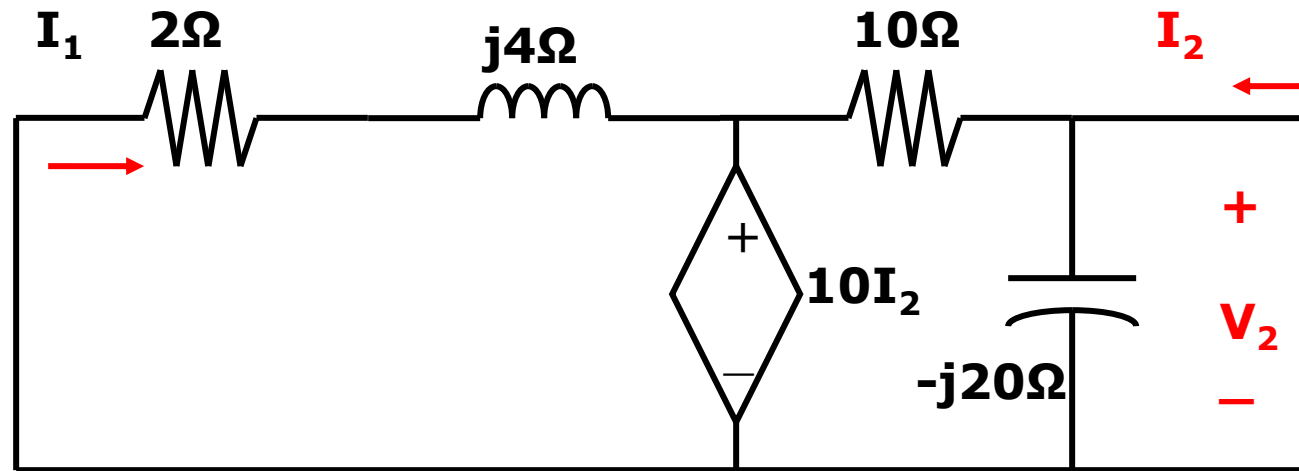ii)  $V_1 = 0$  (short – circuit port 1). Redraw the circuit.



$$I_1 = \frac{-10I_2}{2 + j4} \dots\dots(1)$$

$$I_2 = \frac{V_2}{-j20} + \frac{V_2 - 10I_2}{10}$$

$$2I_2 = V_2 \left( \frac{1}{10} + \frac{1}{-j20} \right) \dots\dots(2)$$

$$\therefore Y_{22} = \frac{I_2}{V_2} = (0.05 + j0.025) \text{ S}$$

sub (2)  $\rightarrow$  (1)

$$Y_{12} = \frac{I_1}{V_2} = (-0.1 + j0.075) \text{ S}$$

In matrix form;


$$\therefore [Y] = \begin{bmatrix} 0.1 + j0.2 & -0.1 + j0.075 \\ 0 & 0.05 + j0.025 \end{bmatrix} \text{ S}$$
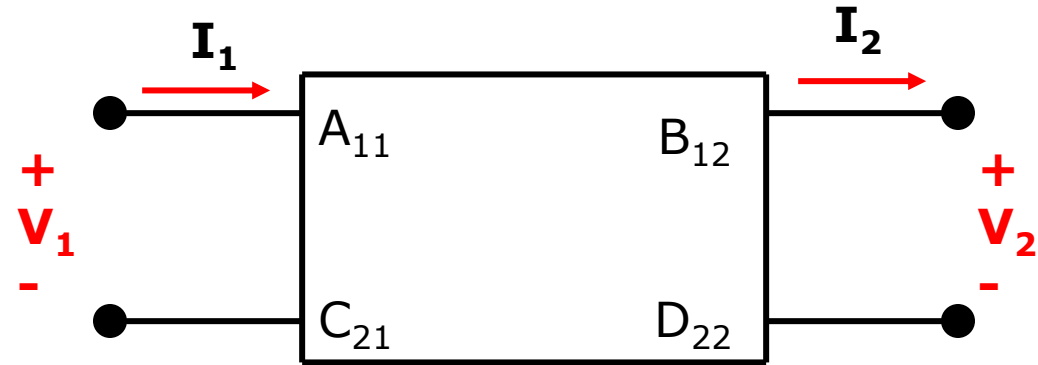
# T (ABCD) PARAMETER

- T – parameter or ABCD – parameter is a another set of parameters relates the variables at the input port to those at the output port.
- T – parameter also called *transmission parameters* because this parameter are useful in the analysis of transmission lines because they express sending – end variables ( $V_1$  and  $I_1$ ) in terms of the receiving – end variables ( $V_2$  and  $-I_2$ ).



- The “black box” that we want to replace with T – parameter is as shown below.



- The equation is:

$$V_1 = AV_2 - BI_2 \dots \dots (1)$$

$$I_1 = CV_2 - DI_2 \dots \dots (2)$$

- In matrix form is:

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

- The T – parameter that we want determine are A, B, C and D where A and D are dimensionless, B is in ohm ( $\Omega$ ) and C is in siemens (S).
- The values can be evaluated by setting
  - i)  $I_2 = 0$  (input port open – circuit)
  - ii)  $V_2 = 0$  (output port short circuit)