



# **VLSI Design (BEC-41)** **(Unit-2, Lecture-3)**



**Presented By:**  
**Prof. R. K. Chauhan**

**Department of Electronics and Communication Engineering**



# Resistive-Load Inverter

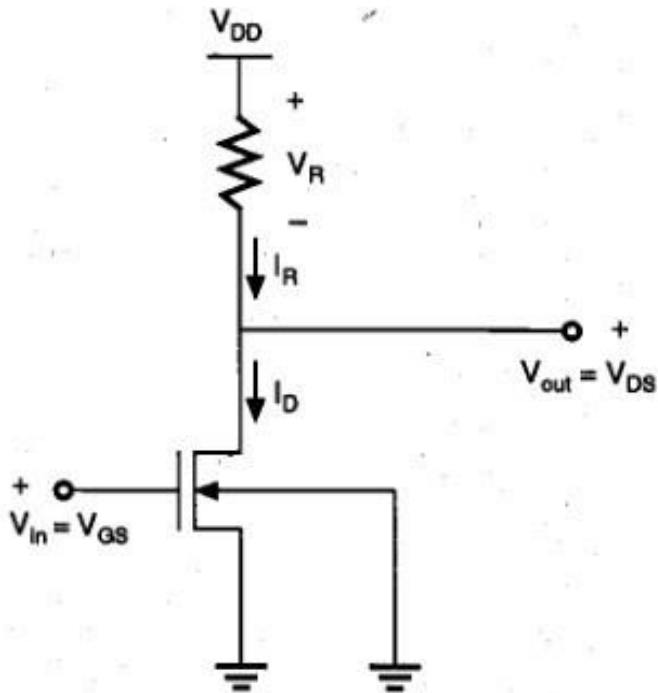



Fig. Resistive load inverter

**Table:** Operating regions of the driver transistor in the resistive-load inverter.

Input Voltage Range	Operating Mode
$V_{in} < V_{T0}$	cut-off
$V_{T0} \leq V_{in} < V_{out} + V_{T0}$	saturation
$V_{in} \geq V_{out} + V_{T0}$	linear



# Resistive-Load Inverter

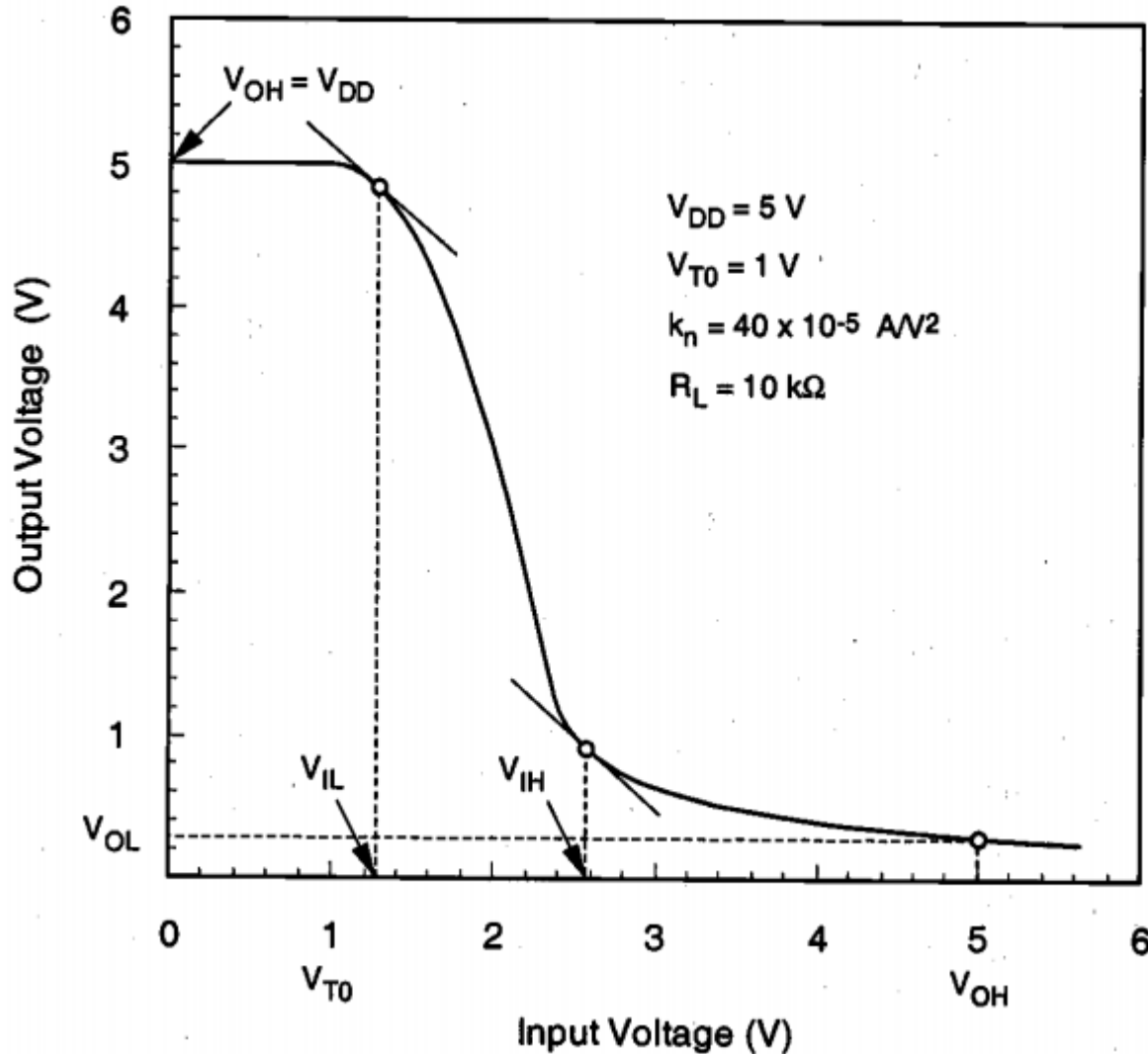

**Fig.** Typical VTC of a resistive-load inverter circuit. Important design parameters of the circuit are shown in the inset.



## Resistive-Load Inverter

### Calculation of $V_{OH}$

- First, we note that the output voltage  $V_{out}$  is given by

$$V_{out} = V_{DD} - R_L \cdot I_R$$

- When the input voltage  $V_{in}$  is low, i.e., smaller than the threshold voltage of the driver MOSFET, the driver transistor is cut-off.
- Since the drain current of the driver transistor is equal to the load current,  $I_R = I_D = 0$ .
- It follows that the output voltage of the inverter under these conditions is:

$$V_{OH} = V_{DD}$$



## Resistive-Load Inverter

### Calculation of $V_{OL}$

- To calculate the output low voltage  $V_{OL}$ , we assume that the input voltage is equal to  $V_{OH}$  i.e.,  $V_{in} = V_{OH} = V_{DD}$ . Since  $V_{in} - V_{T0} > V_{OUT}$  in this case, the driver transistor operates in the linear region. Also note that the load current  $I_R$  is:

$$I_R = \frac{V_{DD} - V_{out}}{R_L}$$

$$\frac{V_{DD} - V_{OL}}{R_L} = \frac{k_n}{2} \cdot \left[ 2 \cdot (V_{DD} - V_{T0}) \cdot V_{OL} - V_{OL}^2 \right]$$

$$V_{OL}^2 - 2 \cdot \left( V_{DD} - V_{T0} + \frac{1}{k_n R_L} \right) \cdot V_{OL} + \frac{2}{k_n R_L} \cdot V_{DD} = 0$$

$$V_{OL} = V_{DD} - V_{T0} + \frac{1}{k_n R_L} - \sqrt{\left( V_{DD} - V_{T0} + \frac{1}{k_n R_L} \right)^2 - \frac{2 V_{DD}}{k_n R_L}}$$



## Resistive-Load Inverter

### Calculation of $V_{IL}$

- By definition,  $V_{IL}$  is the smaller of the two input voltage values at which the slope of the VTC becomes equal to (-1), i.e.,  $dV_{out}/dV_{in} = -1$ .
- Simple inspection of VTC that when the input is equal to  $V_{IL}$ , the output voltage ( $V_{out}$ ) is only slightly smaller than  $V_{OH}$ .
- Consequently,  $V_{out} > V_{in} - V_{T0}$ , and the driver transistor operates in saturation.

$$\frac{V_{DD} - V_{out}}{R_L} = \frac{k_n}{2} \cdot (V_{in} - V_{T0})^2$$

- To satisfy the derivative condition, we differentiate both sides of equation with respect to  $V_{in}$ , which results in the following equation:

$$-\frac{1}{R_L} \cdot \frac{dV_{out}}{dV_{in}} = k_n \cdot (V_{in} - V_{T0}) \qquad V_{IL} = V_{T0} + \frac{1}{k_n R_L}$$



## Resistive-Load Inverter

### Calculation of $V_{IH}$

- $V_{IH}$  is the larger of the two voltage points on VTC at which the slope is equal to (-1).
- When the input voltage is equal to  $V_{IH}$ , the output voltage  $V_{out}$ , is only slightly larger than the output low voltage  $V_{OL}$ .
- Hence,  $V_{out} < V_{in} - V_{T0}$ , and the driver transistor operates in the linear region.

$$\frac{V_{DD} - V_{out}}{R_L} = \frac{k_n}{2} \cdot [2 \cdot (V_{in} - V_{T0}) \cdot V_{out} - V_{out}^2]$$

- Differentiating both sides with respect to  $V_{in}$ , we obtain:

$$-\frac{1}{R_L} \cdot \frac{dV_{out}}{dV_{in}} = \frac{k_n}{2} \cdot \left[ 2 \cdot (V_{in} - V_{T0}) \cdot \frac{dV_{out}}{dV_{in}} + 2 V_{out} - 2 V_{out} \cdot \frac{dV_{out}}{dV_{in}} \right]$$



## Resistive-Load Inverter

### Calculation of $V_{IH}$ (Continued..)

- Next, we can substitute  $dV_{out}/dV_{in} = -1$  into previous equation, since the slope of the VTC is equal to (-1) also at  $V_{in} = V_{IH}$

$$-\frac{1}{R_L} \cdot (-1) = k_n \cdot [(V_{IH} - V_{T0}) \cdot (-1) + 2V_{out}]$$

$$V_{IH} = V_{T0} + 2V_{out} - \frac{1}{k_n R_L}$$


$$\frac{V_{DD} - V_{out}}{R_L} = \frac{k_n}{2} \cdot \left[ 2 \cdot \left( V_{T0} + 2V_{out} - \frac{1}{k_n R_L} - V_{T0} \right) \cdot V_{out} - V_{out}^2 \right]$$

$$V_{out}(V_{in} = V_{IH}) = \sqrt{\frac{2}{3} \cdot \frac{V_{DD}}{k_n R_L}} \quad V_{IH} = V_{T0} + \sqrt{\frac{8}{3} \cdot \frac{V_{DD}}{k_n R_L}} - \frac{1}{k_n R_L}$$





## Resistive-Load Inverter

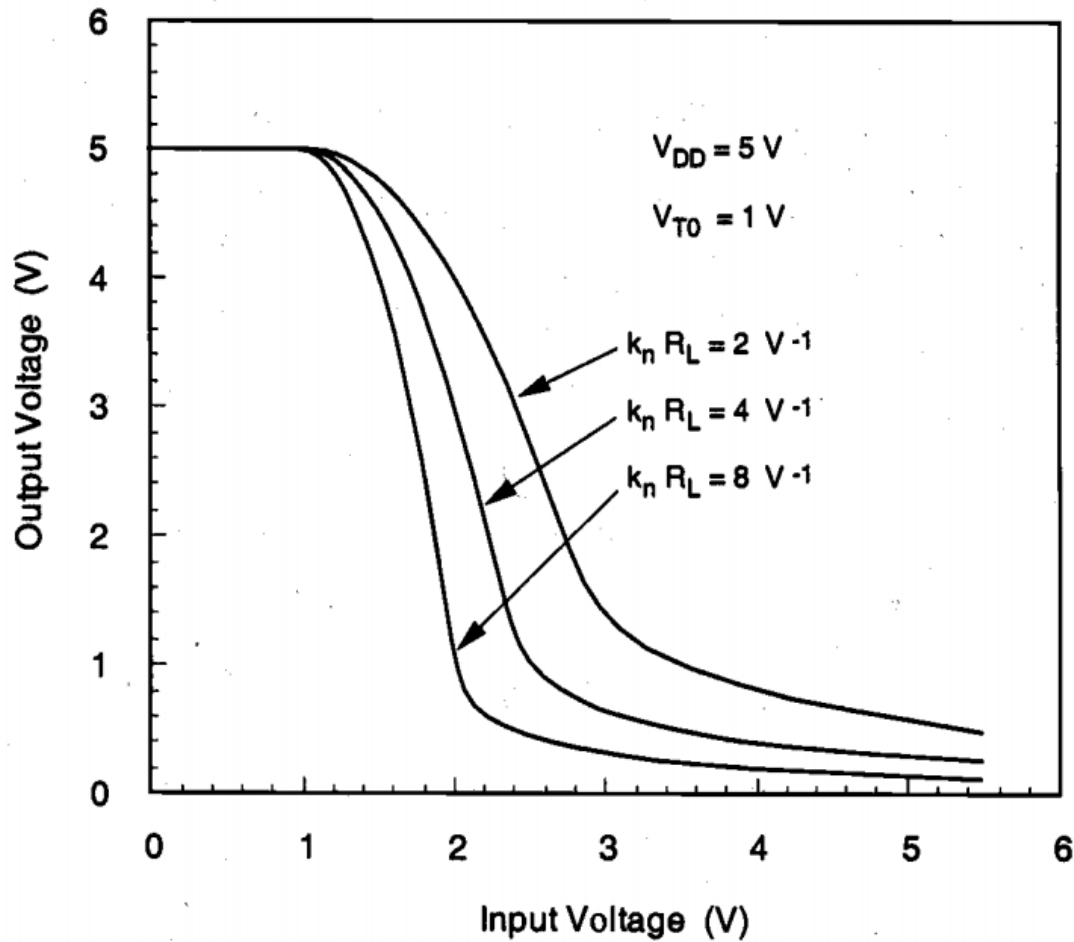

**Fig.** Voltage transfer characteristics of the resistive-load inverter, for different values of the parameter ( $k_n R_L$ )