

ELECTRONIC MEASUREMENT & INSTRUMENTATION (BEC-29)



Instructor
Dr. Brijesh Mishra
Assistant Professor


Department of Electronics and Communication Engineering
Madan Mohan Malaviya University of Technology , Gorakhpur

UNIT-III


Digital to Analog Converters (DAC)

What is a DAC?

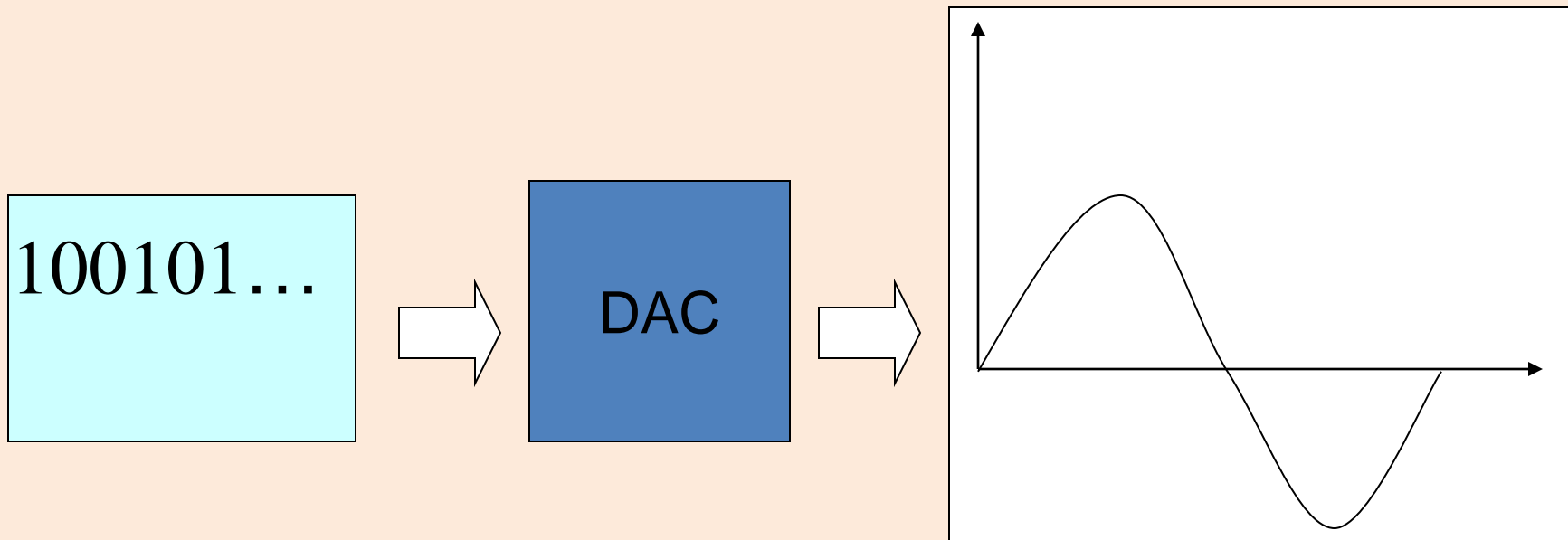- A digital to analog converter (DAC) converts a digital signal to an analog voltage or current output.



What is a DAC?

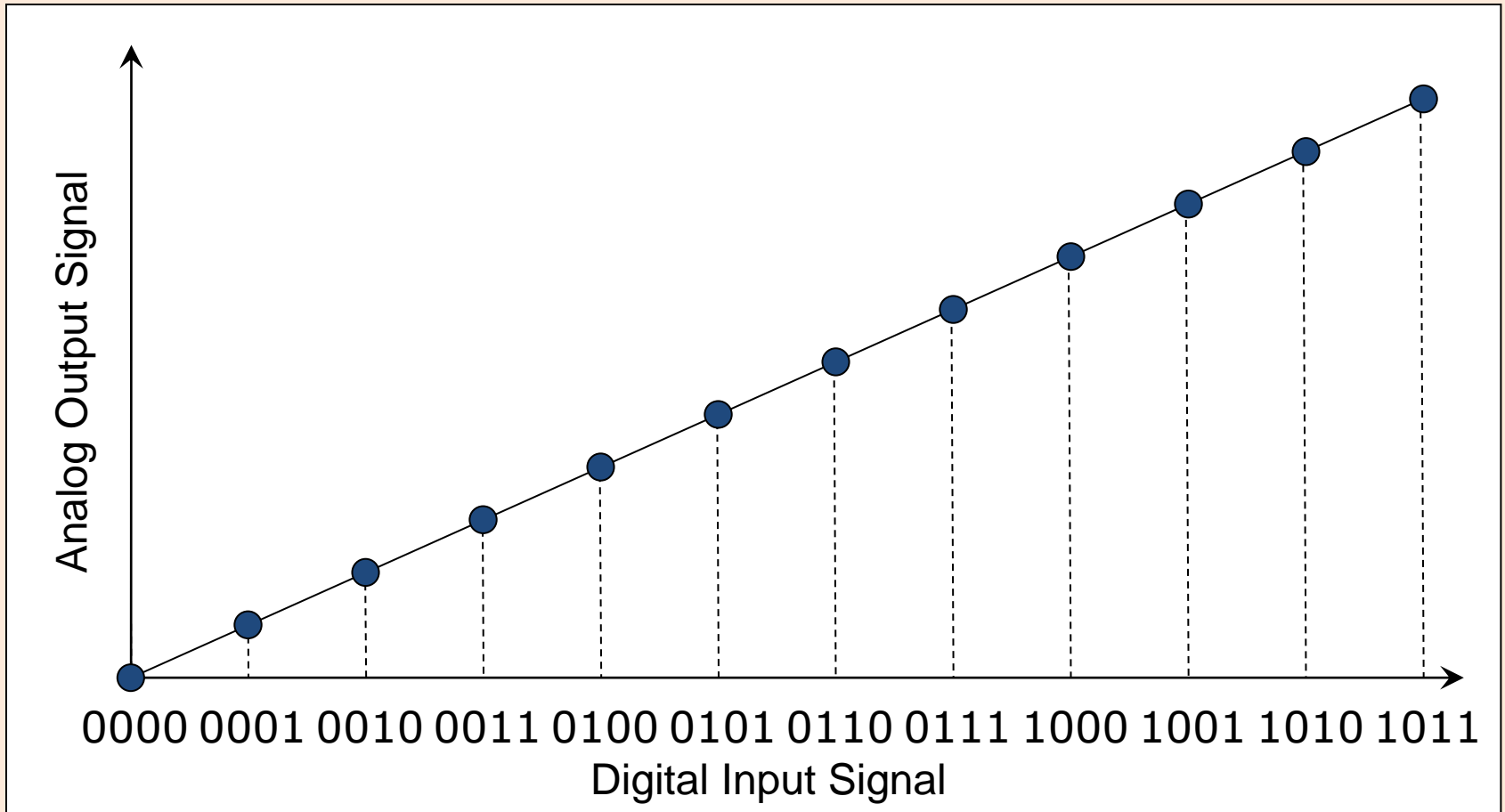

Types of DACs


- Many types of DACs available.
- Usually switches, resistors, and op-amps used to implement conversion
- Two Types:
 - Binary Weighted Resistor
 - R-2R Ladder

Binary Weighted Resistor

- Utilizes a summing op-amp circuit
- Weighted resistors are used to distinguish each bit from the most significant to the least significant
- Transistors are used to switch between V_{ref} and ground (bit high or low)

Binary Weighted Resistor

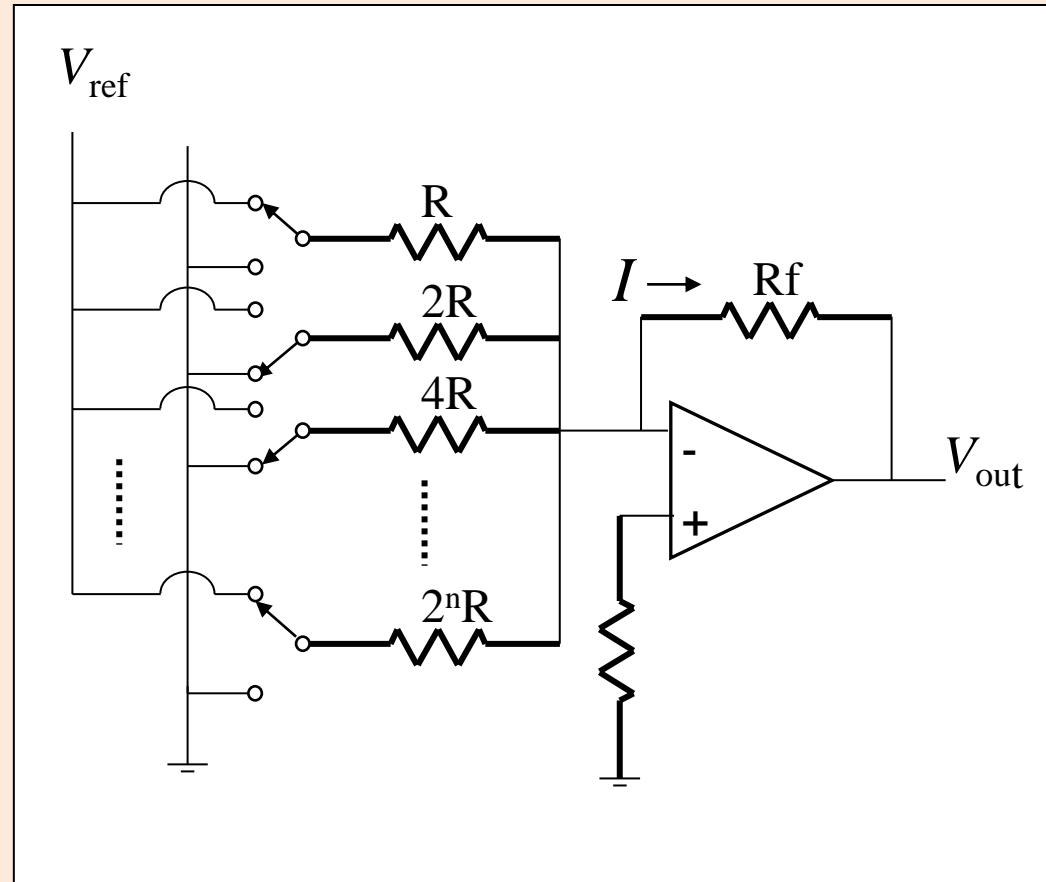- Assume Ideal Op-amp
- No current into op-amp
- Virtual ground at inverting input
- $V_{out} = -IR_f$




Binary Weighted Resistor

Voltages V_1 through V_n are either V_{ref} if corresponding bit is high or ground if corresponding bit is low

V_1 is most significant bit

V_n is least significant bit

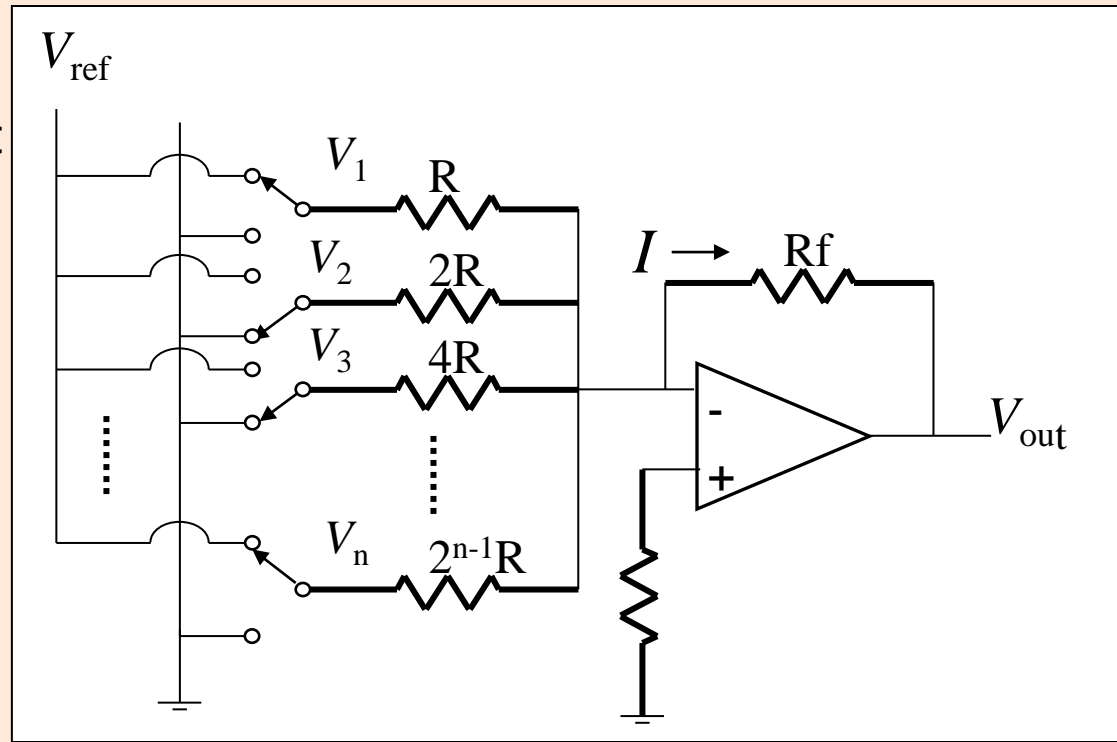

$$V_{out} = -IR_f = -R_f \left(\overset{\text{MSB}}{\frac{V_1}{R}} + \frac{V_2}{2R} + \frac{V_3}{4R} + \dots + \frac{V_n}{2^{n-1}R} \right) \leftarrow \text{LSB}$$

Binary Weighted Resistor

If $R_f = R/2$

$$V_{\text{out}} = -IR_f = -\left(\frac{V_1}{2} + \frac{V_2}{4} + \frac{V_3}{8} + \dots + \frac{V_n}{2^n}\right)$$

For example, a 4-Bit converter yields


$$V_{\text{out}} = -V_{\text{ref}} \left(b_3 \frac{1}{2} + b_2 \frac{1}{4} + b_1 \frac{1}{8} + b_0 \frac{1}{16} \right)$$

Where b_3 corresponds to Bit-3, b_2 to Bit-2, etc.

Binary Weighted Resistor

- Advantages
 - Simple Construction/Analysis
 - Fast Conversion
- Disadvantages
 - Requires large range of resistors (2000:1 for 12-bit DAC) with necessary high precision for low resistors
 - Requires low switch resistances in transistors
 - Can be expensive. Therefore, usually limited to 8-bit resolution.

R-2R Ladder


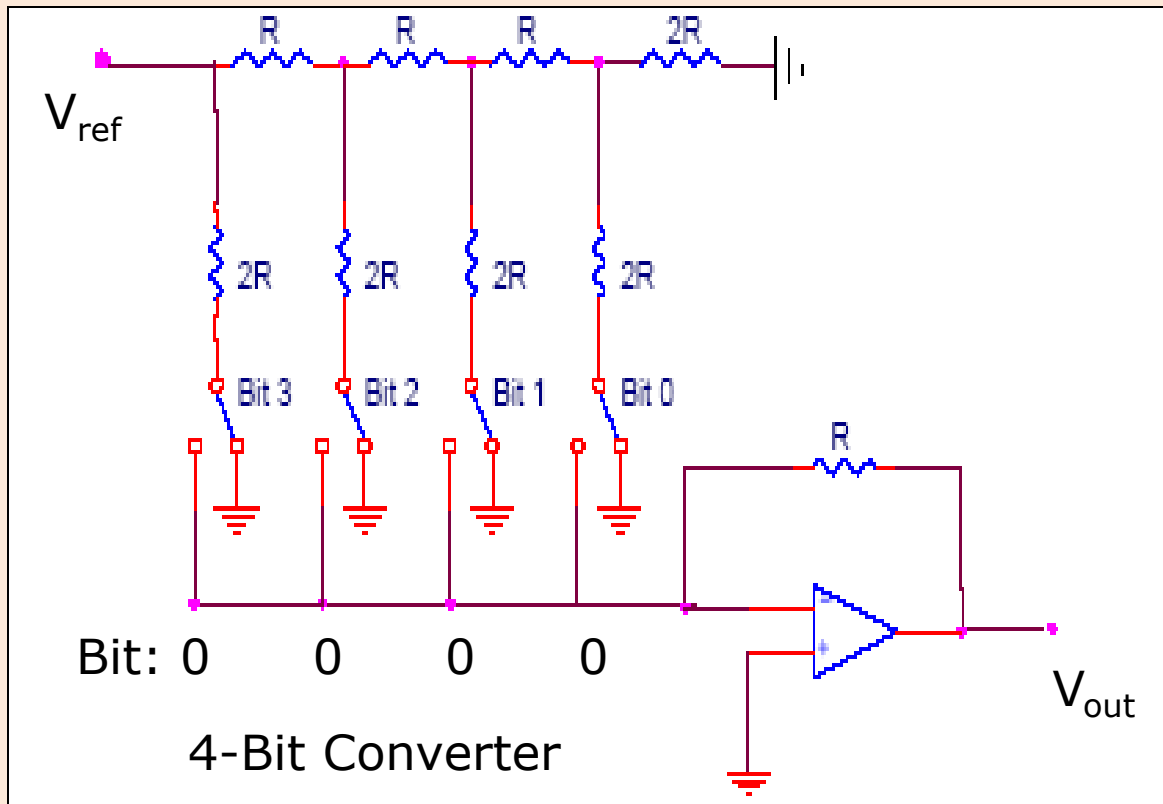


Each bit corresponds to a switch:

If the bit is high, the corresponding switch is connected to the inverting input of the op-amp.



If the bit is low, the corresponding switch is connected to ground.

R-2R Ladder

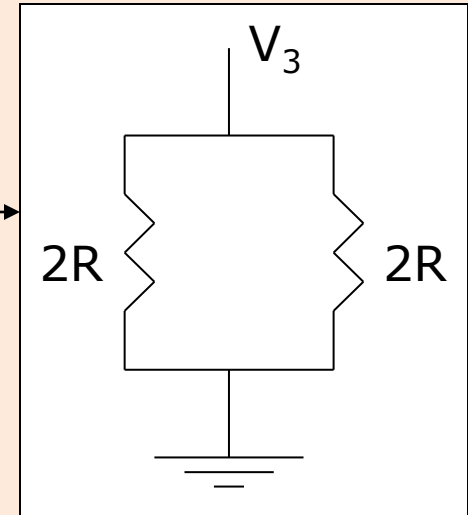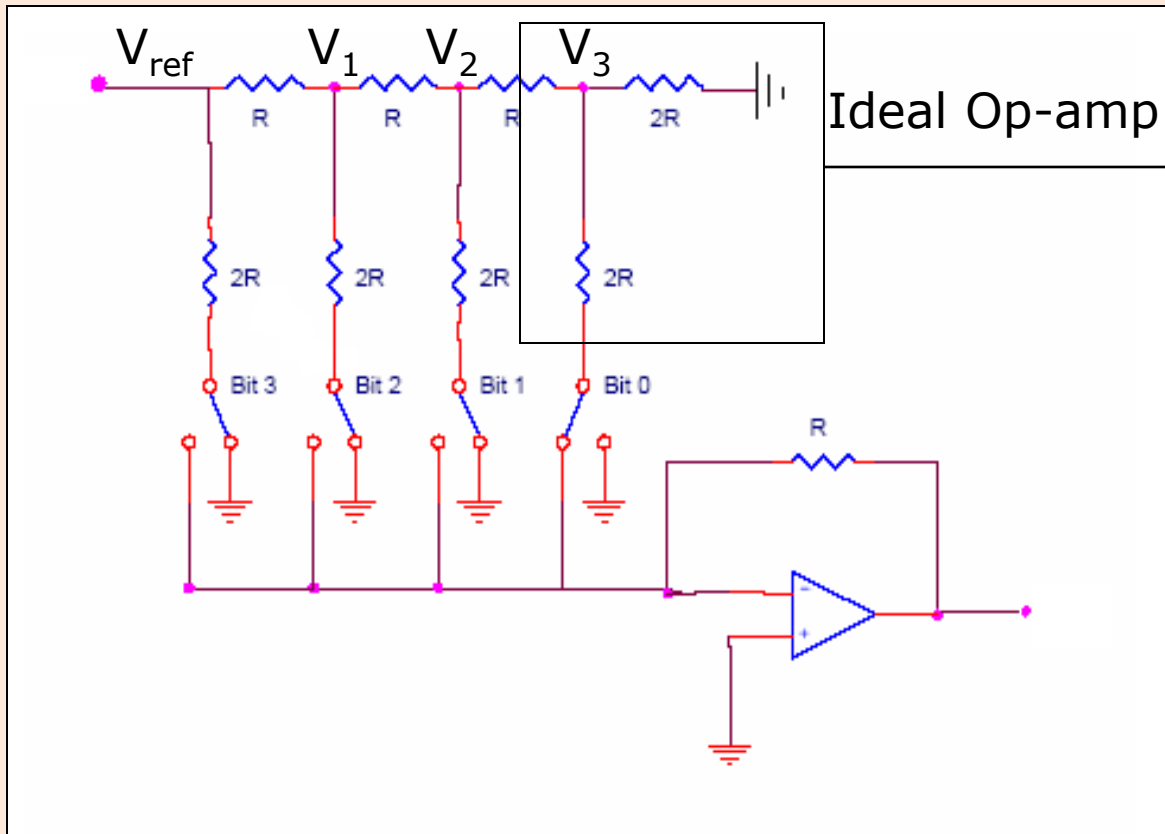

$$R_{eq} = \frac{(2R)(2R)}{(2R + 2R)} = R$$

R-2R Ladder

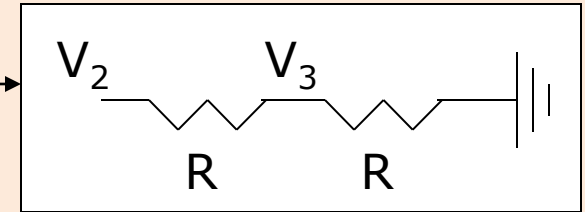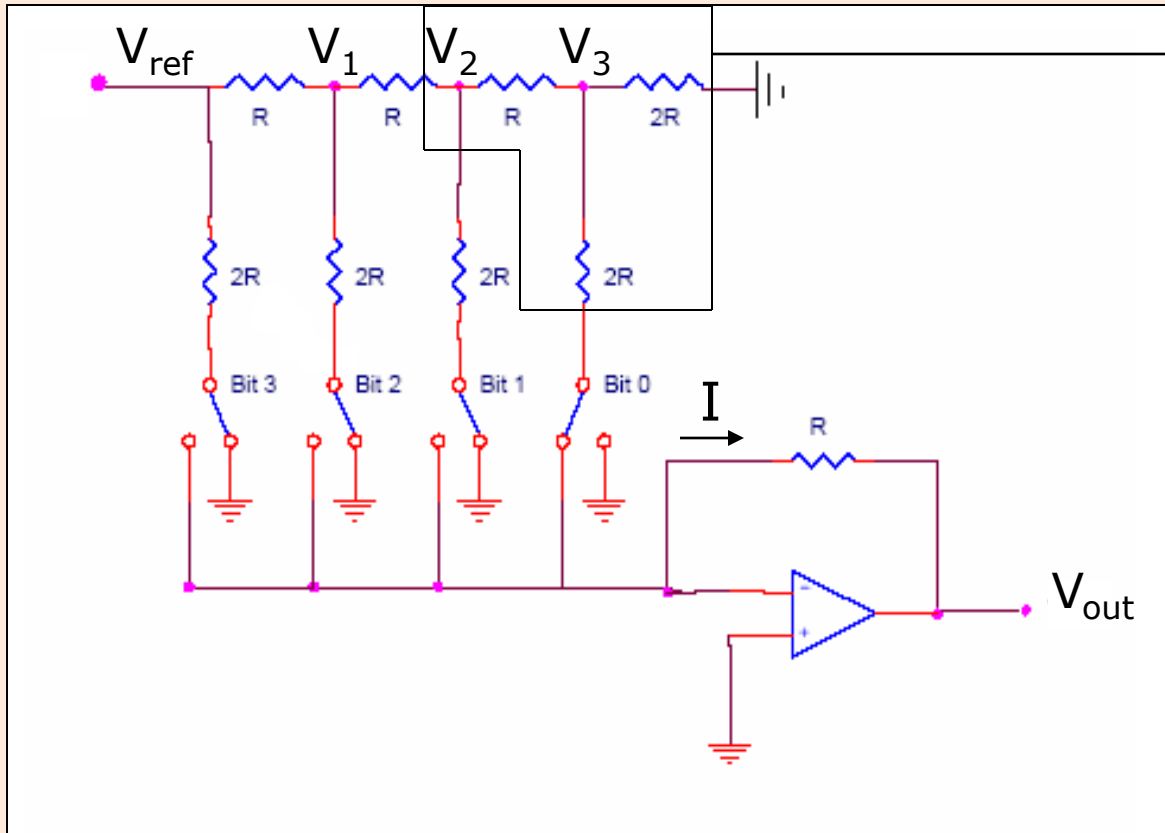

$$V_3 = \left(\frac{R}{R + R} \right) V_2 = \frac{1}{2} V_2$$

Likewise,

$$V_2 = \frac{1}{2} V_1$$

$$V_1 = \frac{1}{2} V_{\text{ref}}$$

$$V_{\text{out}} = -IR$$

R-2R Ladder

Results:


$$V_3 = \frac{1}{8} V_{\text{ref}}, V_2 = \frac{1}{4} V_{\text{ref}}, V_1 = \frac{1}{2} V_{\text{ref}}$$

$$V_{\text{out}} = -R \left(b_3 \frac{V_{\text{ref}}}{2R} + b_2 \frac{V_{\text{ref}}}{4R} + b_1 \frac{V_{\text{ref}}}{8R} + b_0 \frac{V_{\text{ref}}}{16R} \right)$$

Where b_3 corresponds to bit 3, b_2 to bit 2, etc.

If bit n is set, $b_n=1$

If bit n is clear, $b_n=0$

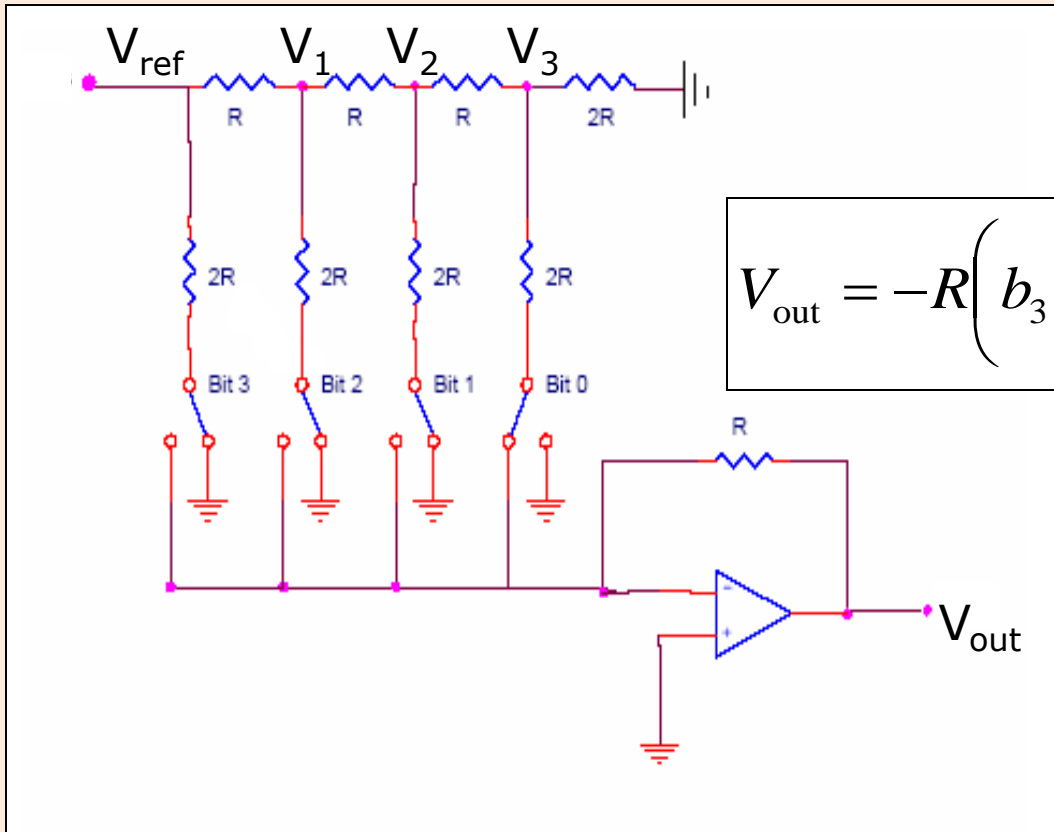

R-2R Ladder

For a 4-Bit R-2R Ladder

$$V_{\text{out}} = -V_{\text{ref}} \left(b_3 \frac{1}{2} + b_2 \frac{1}{4} + b_1 \frac{1}{8} + b_0 \frac{1}{16} \right)$$

For general n-Bit R-2R Ladder or Binary Weighted Resister DAC

$$V_{\text{out}} = -V_{\text{ref}} \sum_{i=1}^n b_{n-i} \frac{1}{2^i}$$

R-2R Ladder

- Advantages
 - Only two resistor values (R and $2R$)
 - Does not require high precision resistors
- Disadvantage
 - Lower conversion speed than binary weighted DAC

Specifications of DACs

- Resolution
- Speed
- Linearity
- Settling Time
- Reference Voltages
- Errors

Resolution

- Smallest analog increment corresponding to 1 LSB change
- An N-bit resolution can resolve 2^N distinct analog levels
- Common DAC has a 8-16 bit resolution

$$\text{Resolution} = V_{LSB} = \frac{V_{ref}}{2^N}$$


where $N = \text{number of bits}$

Speed

- Rate of conversion of a single digital input to its analog equivalent
- Conversion rate depends on
 - clock speed of input signal
 - settling time of converter
- When the input changes rapidly, the DAC conversion speed must be high.

Linearity

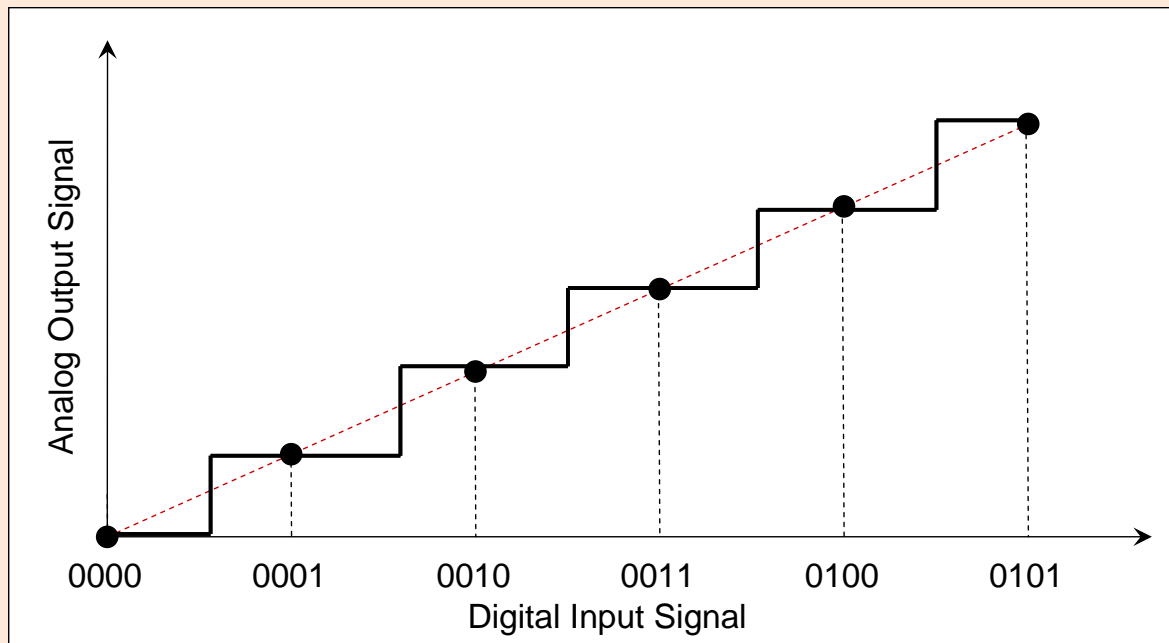
- The difference between the desired analog output and the actual output over the full range of expected values




Linearity

- Ideally, a DAC should produce a linear relationship between the digital input and analog output

Linearity (Ideal)

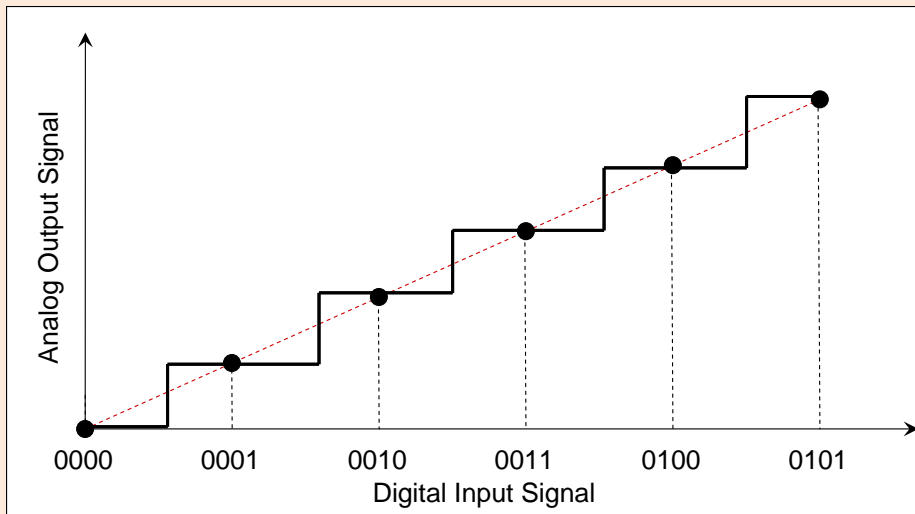


Non-Linearity

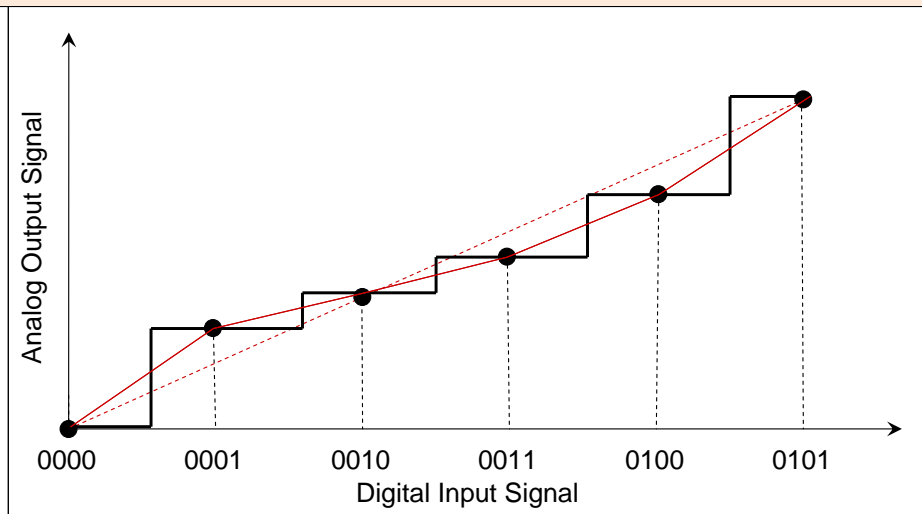

Settling Time

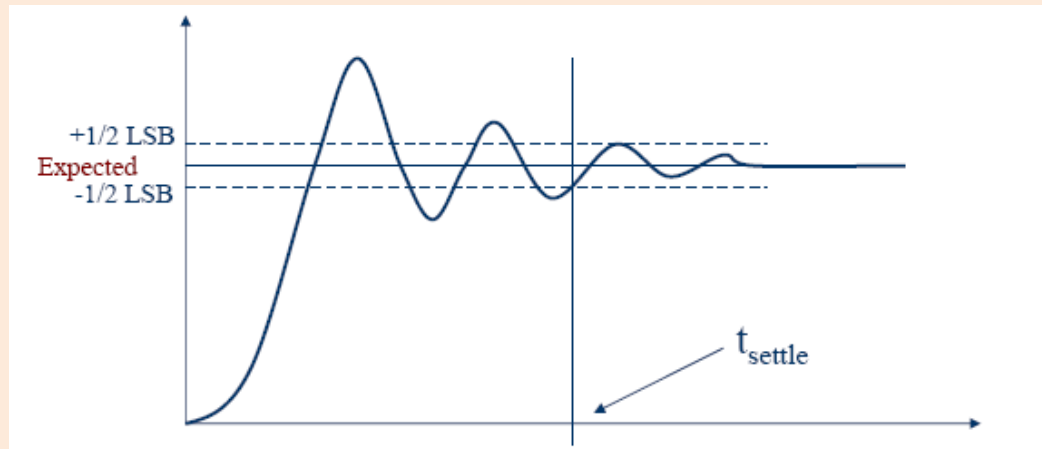- Time required for the output signal to settle within $\pm 1/2$ LSB of its final value after a given change in input scale
- Limited by slew rate of output amplifier
- Ideally, an instantaneous change in analog voltage would occur when a new binary word enters into DAC



Reference Voltages


- Used to determine how each digital input will be assigned to each voltage division
- Types:
 - Non-multiplier DAC: V_{ref} is fixed
 - Multiplier DAC: V_{ref} provided by external source

Types of Errors Associated with DACs

- Gain
- Offset
- Full Scale
- Resolution
- Non-Linearity
- Non-Monotonic
- Settling Time and Overshoot


Gain Error

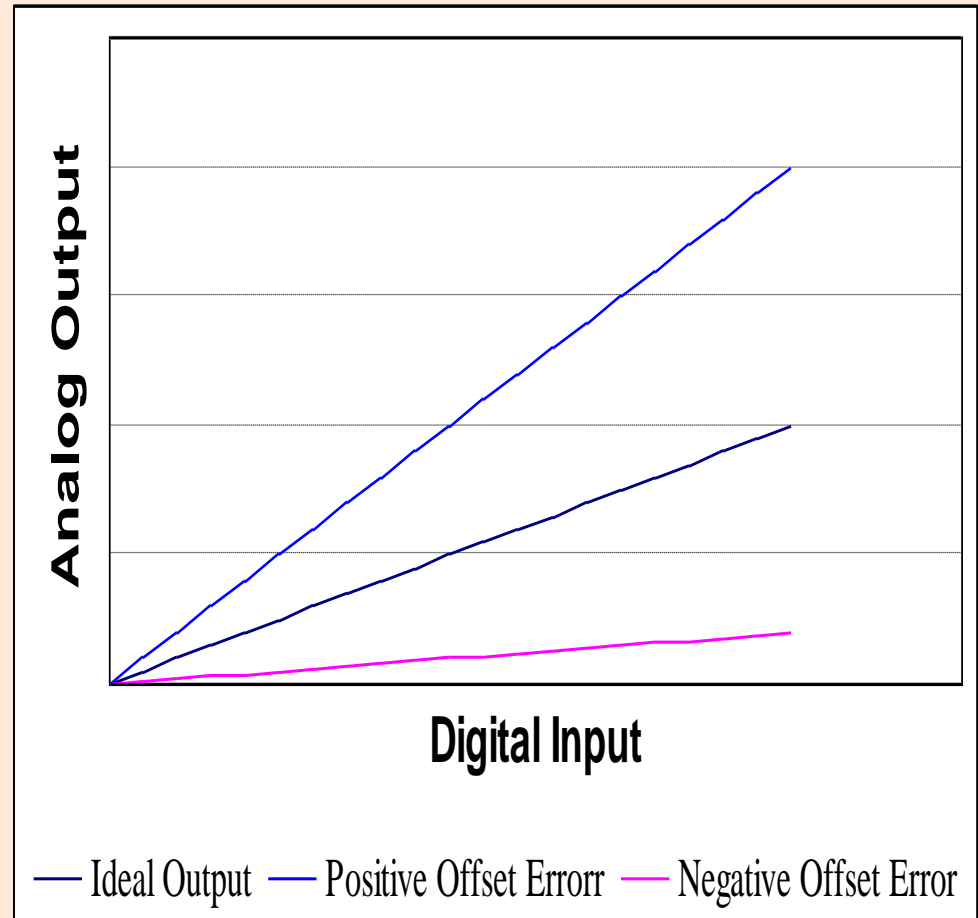- Occurs when the slope of the actual output deviates from the ideal output




Offset Error

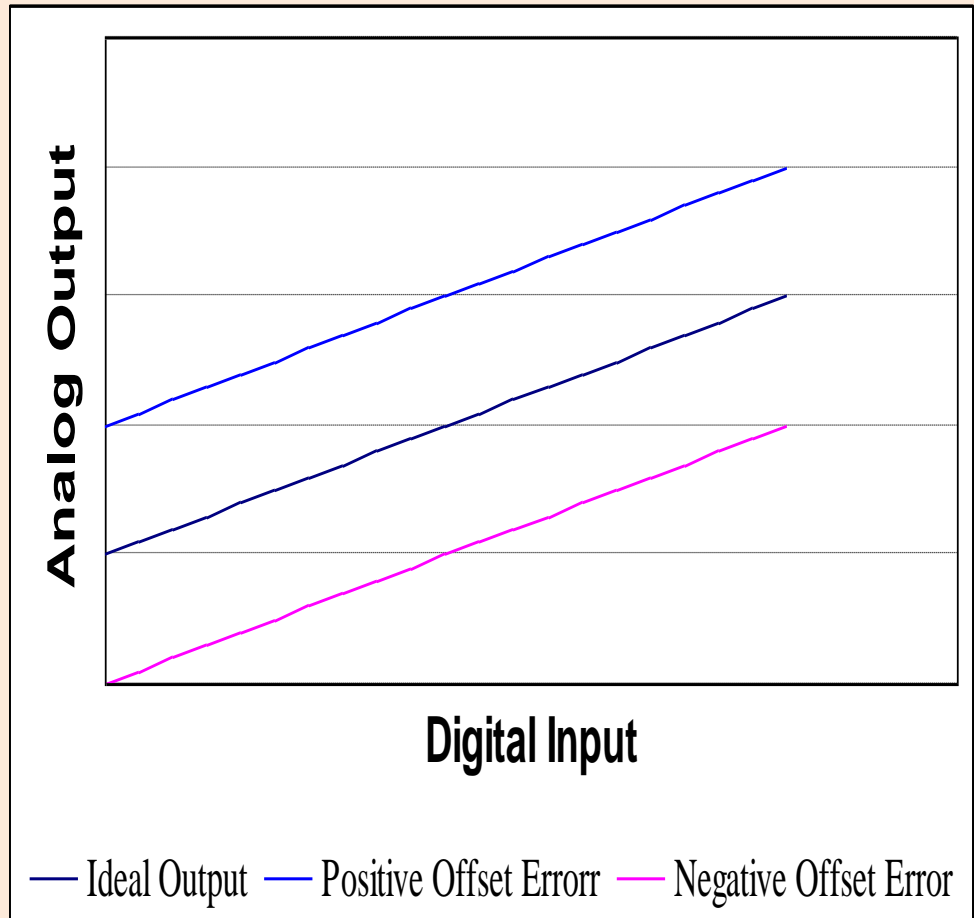- Occurs when there is a constant offset between the actual output and the ideal output




Full Scale Error

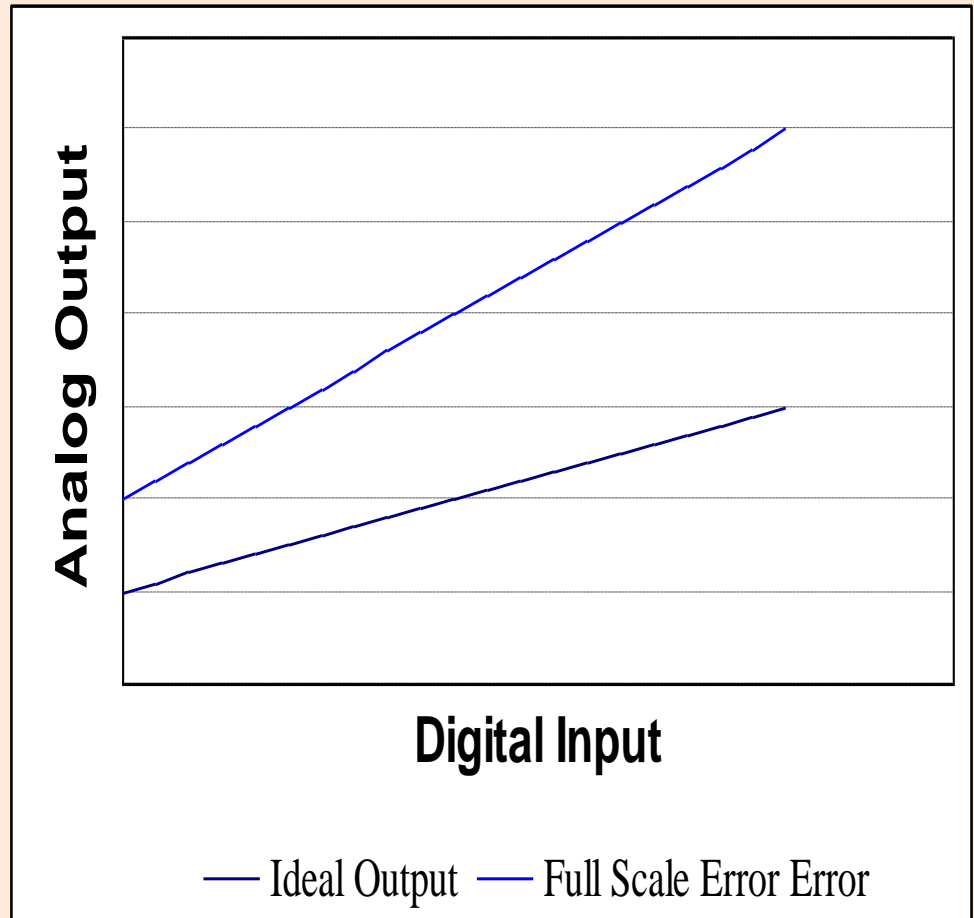- Occurs when the actual signal has both gain and offset errors



Resolution Error

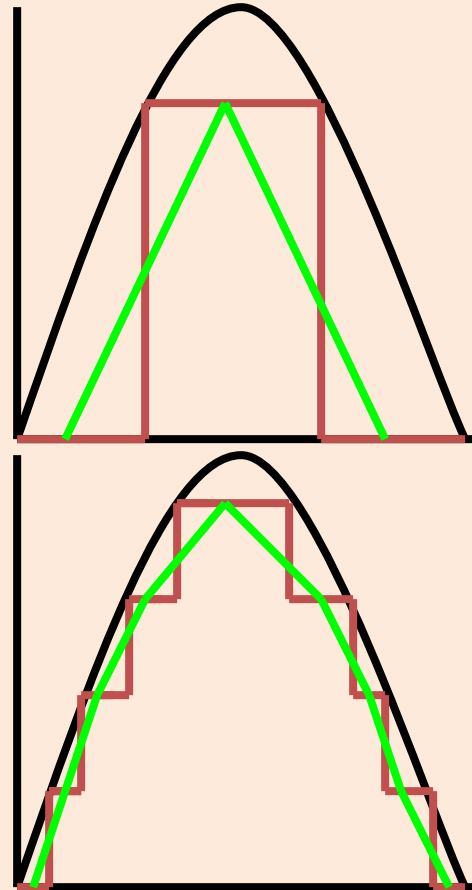
- Poor representation of ideal output due to poor resolution
- Size of voltage divisions affect the resolution



Non-Linearity Error


- Occurs when analog output of signal is non-linear
- Two Types
 - Differential – analog step-sizes changes with increasing digital input (measure of largest deviation; between successive bits)
 - Integral – amount of deviation from a straight line after offset and gain errors removed; on concurrent bits

Non-Linearity Error, cont.

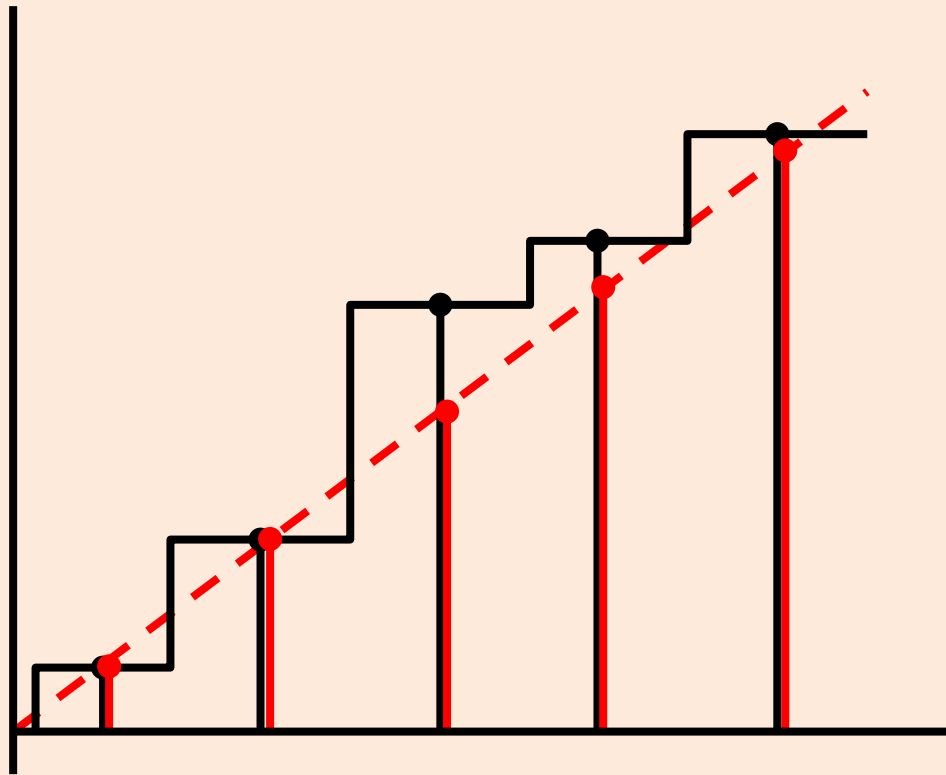


Non-Monotonic Error

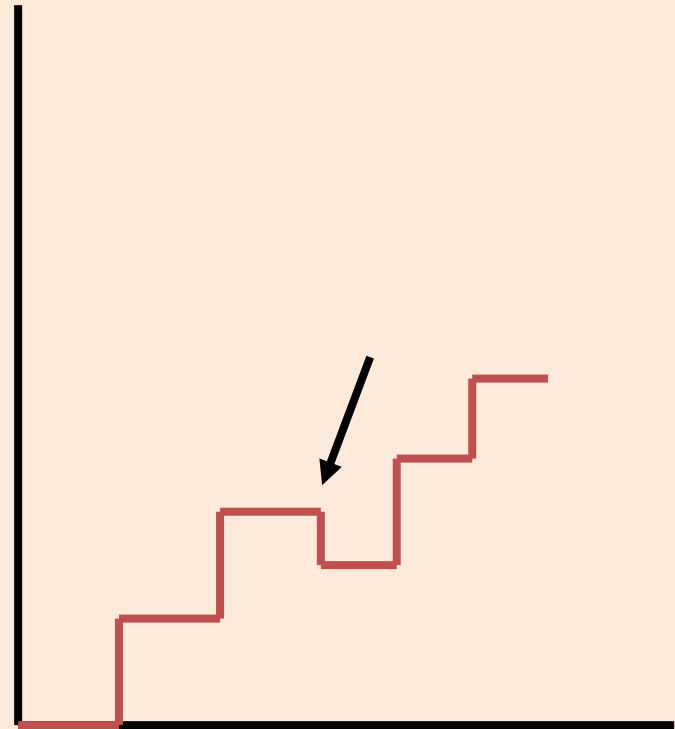- Occurs when an increase in digital input results in a decrease in the analog output



Settling Time and Overshoot Error

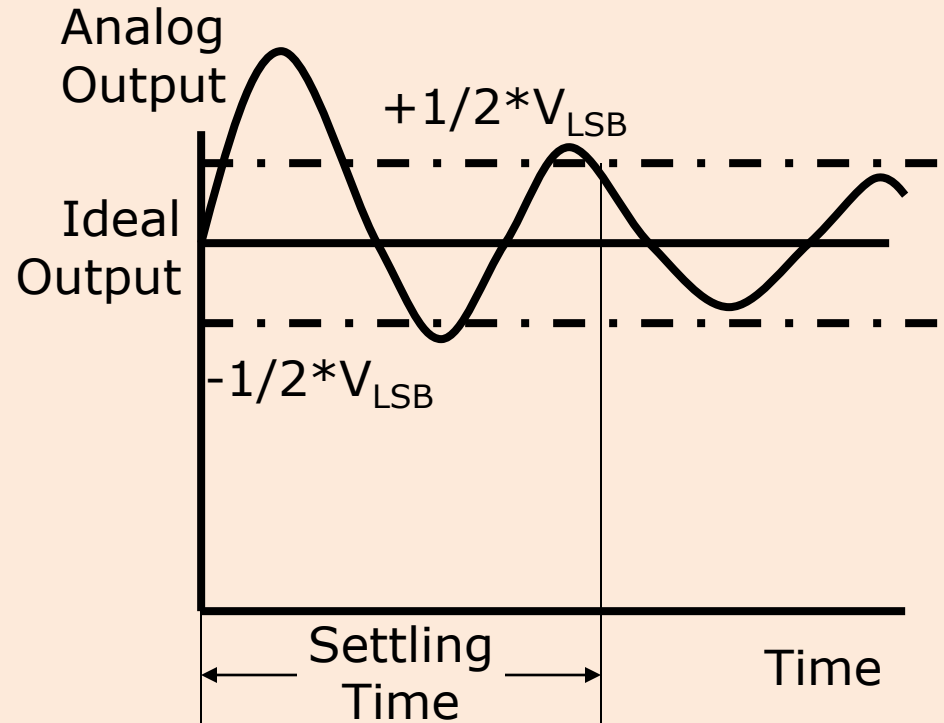- Settling Time – time required for the output to fall within $\pm \frac{1}{2} V_{\text{LSB}}$
- Overshoot – occurs when analog output overshoots the ideal output



Applications

- Digital Motor Control
- Computer Printers
- Sound Equipment (e.g. CD/MP3 Players, etc.)
- Electronic Cruise Control
- Digital Thermostat

References

- Callis, J. B. “The Digital to Analog Converter.” 2002.
http://courses.washington.edu/jbcallis/lectures/C464_Lec5_Sp-02.pdf. 14 March 2006
- “DAC.” 2006. http://en.wikipedia.org/wiki/Digital-to-analog_converter#DAC_types. 14 March 2006.
- Johns, David and Ken Martin. “Data Converter Fundamentals.” © 1997.
http://www.eecg.toronto.edu/~kphang/ece1371/chap11_slides.pdf. 14 March 2006
- Goericke, Fabian, Keunhan Park and Geoffrey Williams. “Digital to Analog Converter.” © 2005.
http://www.me.gatech.edu/mechatronics_course/DAC_F05.ppt. 14 March 2006

THANK YOU