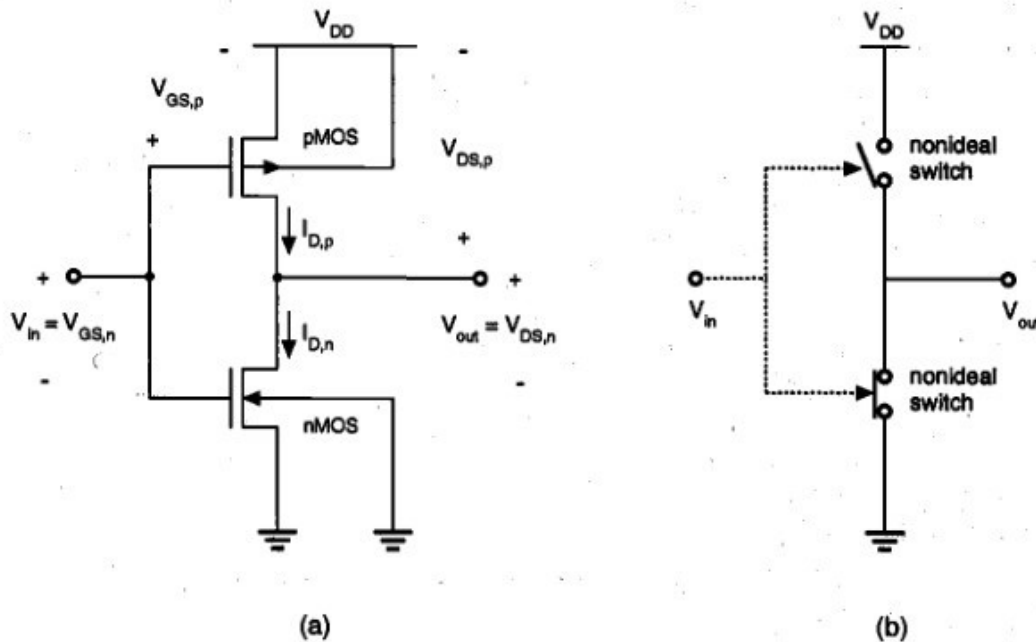


## 4. CMOS Inverter


The CMOS inverter has two important advantages over the other inverter configurations.

The first and perhaps the most important advantage is that the steady-state power dissipation of the CMOS inverter circuit is virtually negligible, except for small power dissipation due to leakage currents. In all other inverter structures examined so far, a nonzero steady-state current is drawn from the power source when the driver transistor is turned on, which results in a significant DC power consumption.

The other advantages of the CMOS configuration are that the voltage transfer characteristic (VTC) exhibits a full output voltage swing between 0 V and  $V_{DD}$ , and that the VTC transition is usually very sharp. Thus, the VTC of the CMOS inverter resembles that of an ideal inverter.



## VTC Characteristic:

 

- A : P Lin N Off
- B : P Lin N Sat
- C : P sat N Sat
- D : P Sat N Lin
- E : Poff N Lin


$$\frac{k_n}{k_p} = \frac{\mu_n C_{ox} \cdot \left(\frac{W}{L}\right)_n}{\mu_p C_{ox} \cdot \left(\frac{W}{L}\right)_p} = \frac{\mu_n \cdot \left(\frac{W}{L}\right)_n}{\mu_p \cdot \left(\frac{W}{L}\right)_p}$$

For Symmetric Inverter  $V_{t0} = V_{t0n} = -V_{t0p} : K_R = 1$

$$\frac{\left(\frac{W}{L}\right)_n}{\left(\frac{W}{L}\right)_p} = \frac{\mu_p}{\mu_n} \approx \frac{230 \text{ cm}^2/\text{V}\cdot\text{s}}{580 \text{ cm}^2/\text{V}\cdot\text{s}}$$

$$\left(\frac{W}{L}\right)_p \approx 2.5 \left(\frac{W}{L}\right)_n$$

## MOS Combinational Circuit

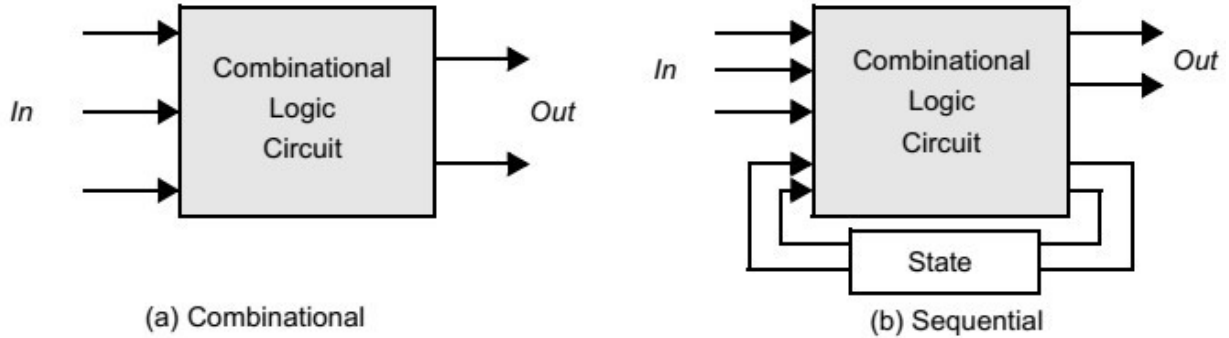

High level classification of logic circuits.

### **Different Logic Families:**

1. **Static CMOS Design**
  - a. Complementary CMOS
  - b. Ratioed Logic
  - c. Pass-Transistor Logic
2. **Dynamic CMOS Design**
  - a. Domino logic
  - b. NORA logic
  - c. Zipper CMOS Circuits